

TSTE26 Powergrid and technology for renewable
production

Lecture 2

Photo Voltaic – solar generator systems

Lars Eriksson
FS/ISY

Outline

- PV Cell Modeling 2
- Shading
- Module configuration
- DC/DC conversion
- MPPT
- Grid connection

Solar module configuration

Understanding array configurations

- PV-cell characteristics
- Parallel, series connection
- Bypass diodes
- Shading


The PV-cell

Solar-cell defined with generator references


Current direction out of the cell

Only 1st quadrant used


Generator reference-arrow system:

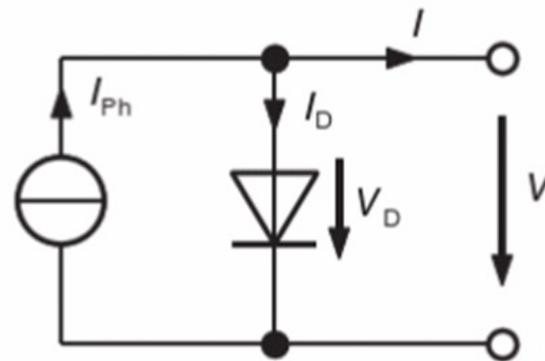



Characteristic curve:

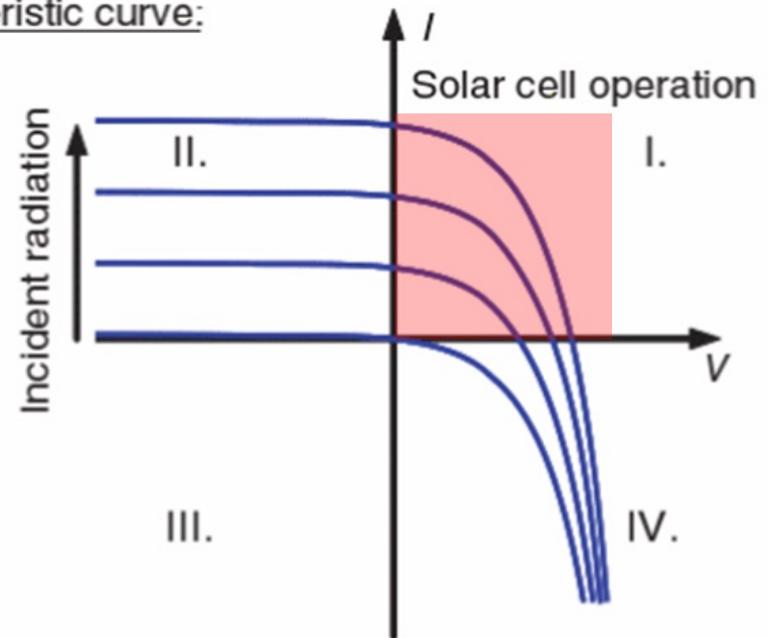

Solar cell symbol:

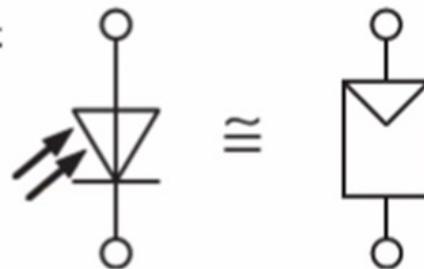

IV-characteristics

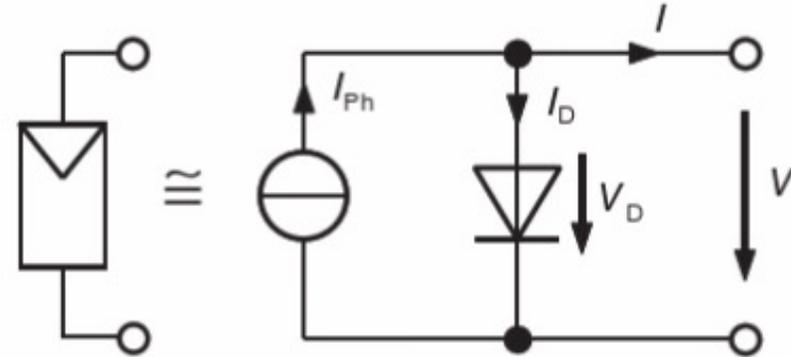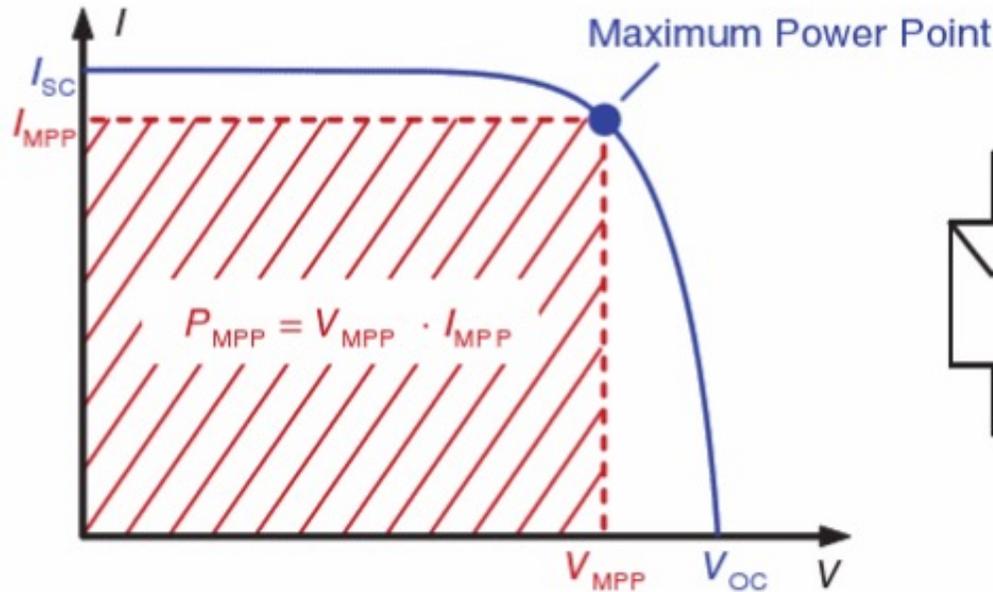

Shockley diode equation

$$I = I_{Ph} - I_D = I_{Ph} - I_S \cdot \left(e^{\frac{m \cdot V}{V_T}} - 1 \right)$$

$$V_T = \frac{kT}{q} = 25.9 \text{ mV (thermal voltage)}$$

m ideality factor ($1 < m < 2$)


Short circuit current

$$I_{SC} = I(V=0) = I_{Ph} - I_S \cdot (e^0 - 1) = I_{Ph}$$

Open circuit voltage

$$V_{OC} = V(I=0) = m \cdot V_T \cdot \ln \left(\frac{I_{SC}}{I_S} + 1 \right)$$

Maximum Power Point


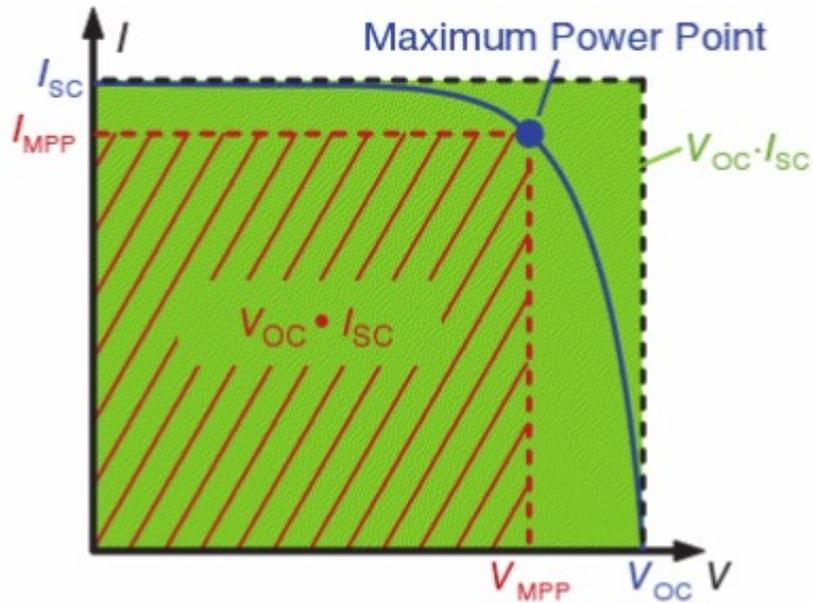


- Fill Factor

$$FF = \frac{V_{MPP} \cdot I_{MPP}}{V_{OC} \cdot I_{SC}} = \frac{P_{MPP}}{V_{OC} \cdot I_{SC}}$$


- Efficiency
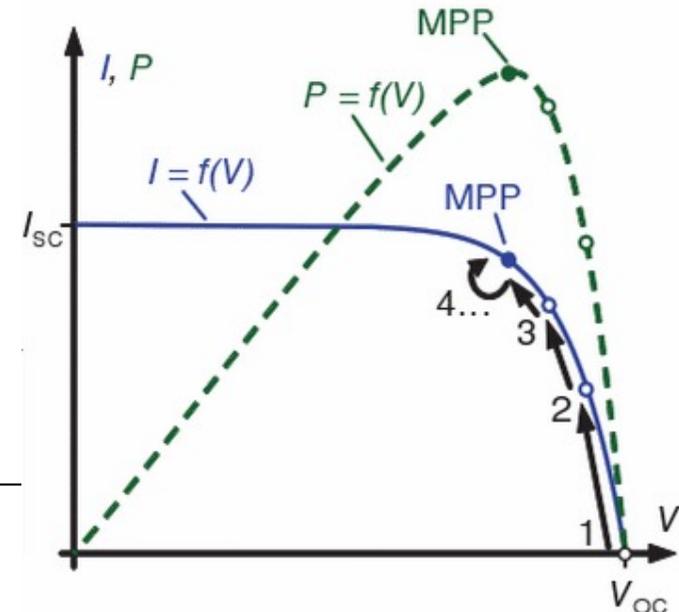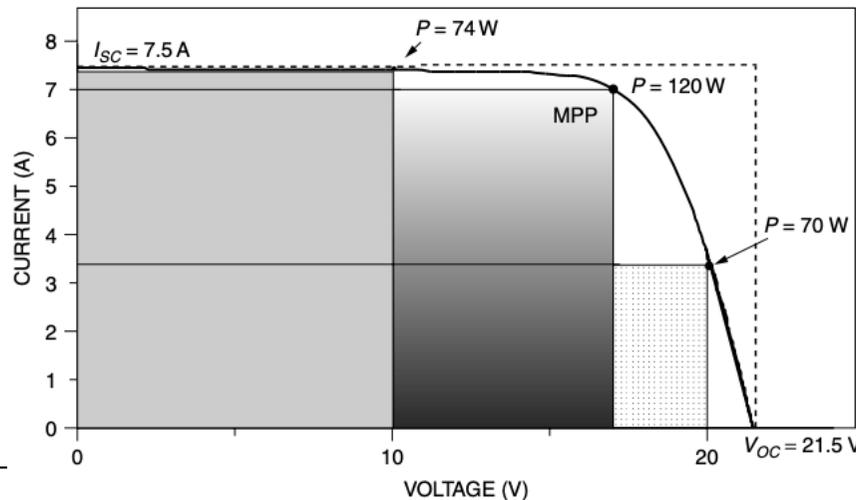
$$\eta = \frac{P_{MPP}}{P_{Opt}} = \frac{P_{MPP}}{E \cdot A} = \frac{FF \cdot V_{OC} \cdot I_{SC}}{E \cdot A}$$




Step 1 - Diode equationen

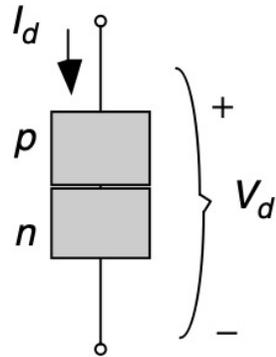
- Characteristics for Diode: Shockley Equation $I_d = I_0 \left(e^{\frac{k}{qT} V_d} - 1 \right)$
 - k – Boltzmann's konstant ($1.381 \cdot 10^{-23} \text{ J/K}$)
 - q – Elementary charge ($1.602 \cdot 10^{-19} \text{ C}$)
 - I_0 – Reverse saturation current ($\sim 10^{-12} \text{ A/cm}^2$)
 - 25°C conditions, $\frac{k}{qT} = 38.9 = \frac{1}{25.7 \cdot 10^{-3}} = \frac{1}{V_T}$



(a) p - n junction diode

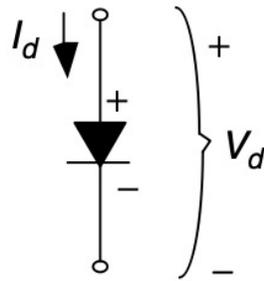

(b) Symbol for real diode

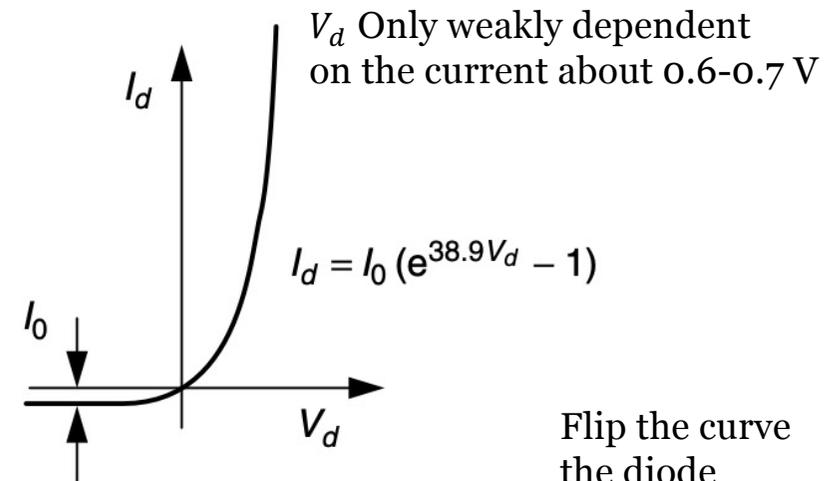




(c) Diode characteristic curve

Step 2a: Current source + Diode equation


Current I_{SC} is determined by irradiation and the diode steals current

$$I = I_{SC} - I_d$$
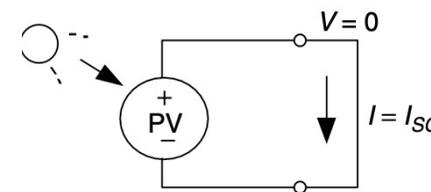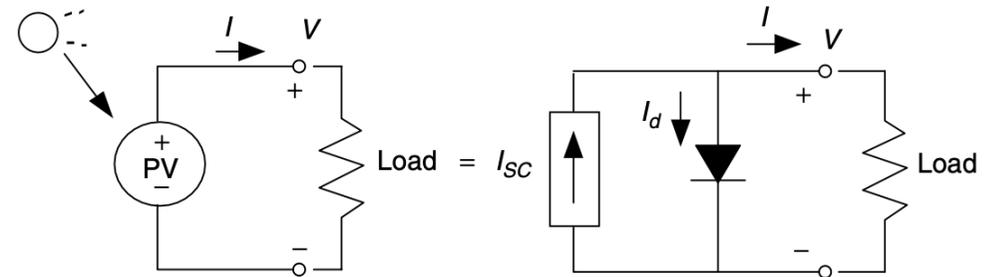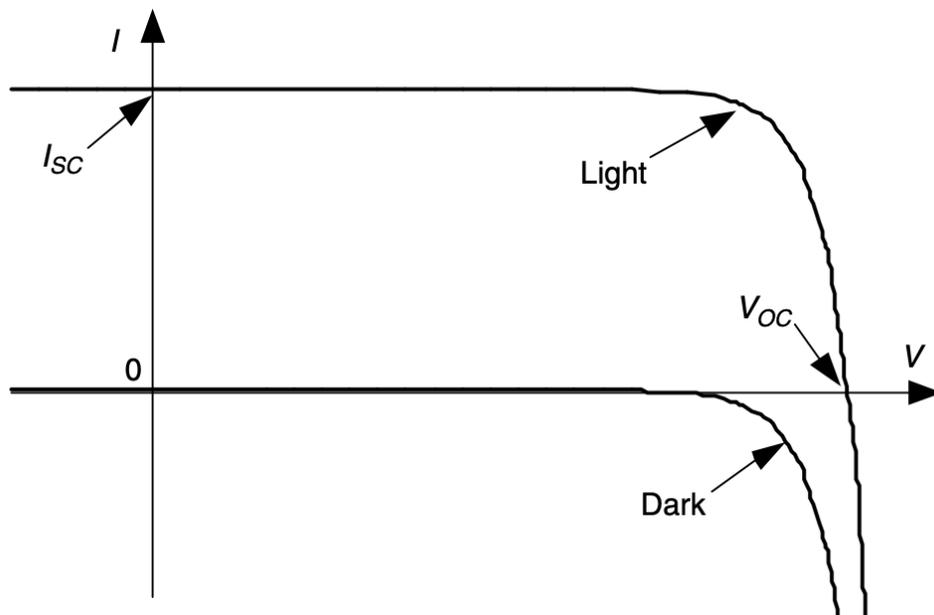
$$I = I_{SC} - I_0 \left(e^{\frac{k}{qT} V_d} - 1 \right)$$



(a) Short-circuit current

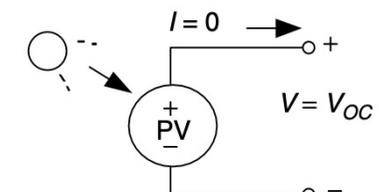

(b) Open-circuit voltage


No Power delivery at the extreme points.
-Vill veta vad vi får ut mellan extremerna

Step 2b: Current source + Diode equation

Current I_{SC} is determined by irradiation

$$I = I_{SC} - I_d$$
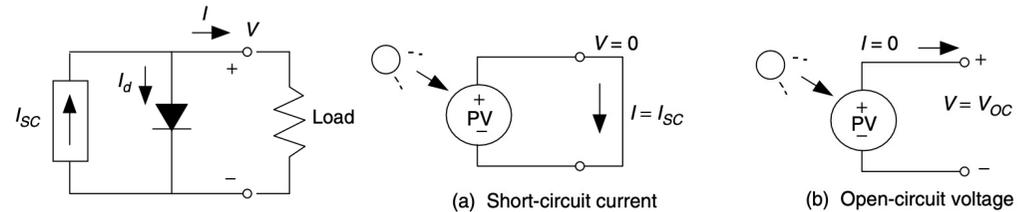
$$I = I_{SC} - I_0 \left(e^{\frac{k}{qT} V_d} - 1 \right)$$




Solve for V_{OC} , $I = 0$

$$V_{OC} = \frac{kT}{q} \ln \left(\frac{I_{SC}}{I_0} + 1 \right)$$

at 25° we get

$$I = I_{SC} - I_0 (e^{38.9 V_d} - 1)$$
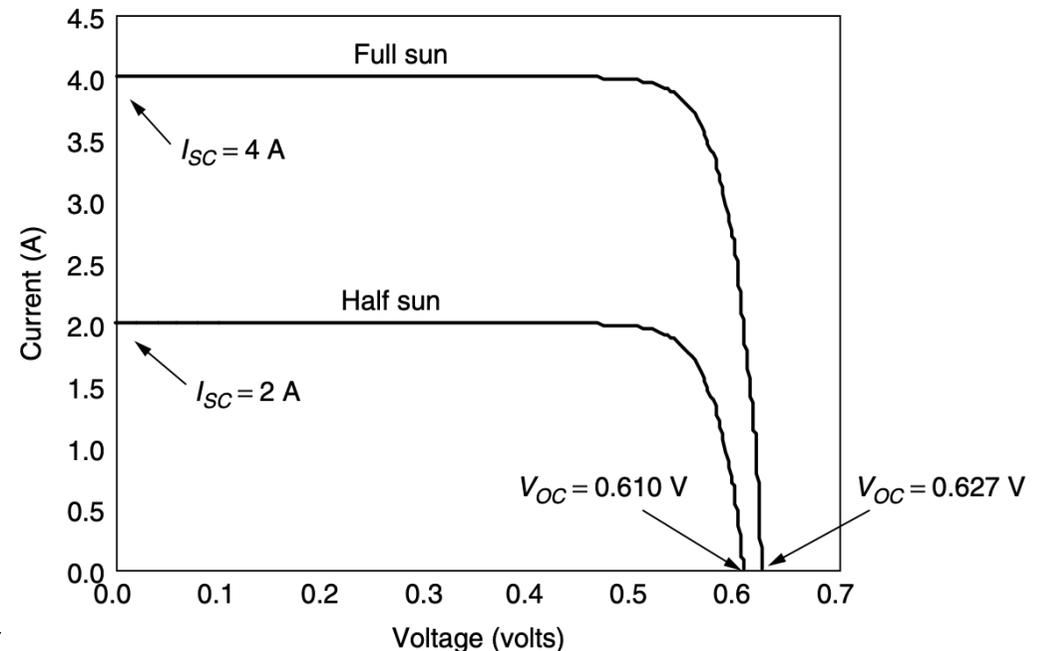
$$V_{OC} = 0.0257 \ln \left(\frac{I_{SC}}{I_0} + 1 \right)$$



Step 3: More complete cell description

- Need two elements more
 - Shaded cell $I_{SC} = 0$
 - Diode blocks
 - Current goes through R_P
 - Resistive series loss R_S


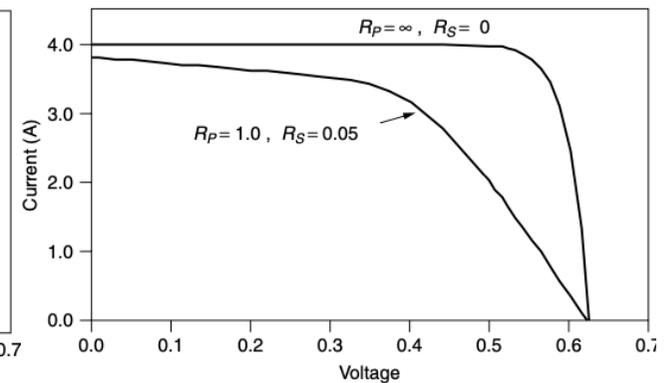
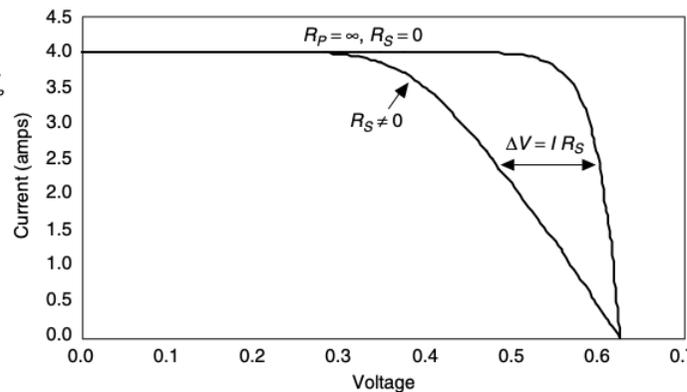
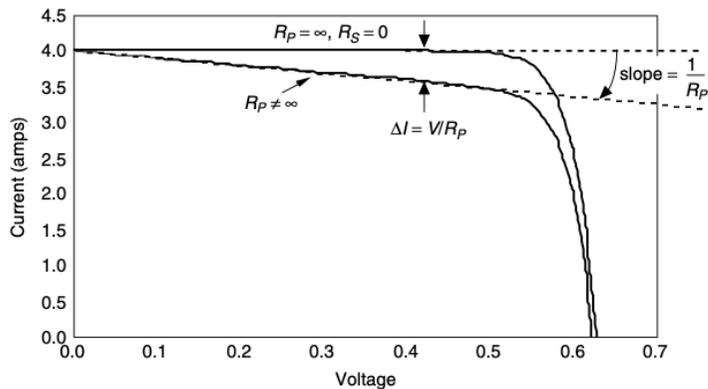
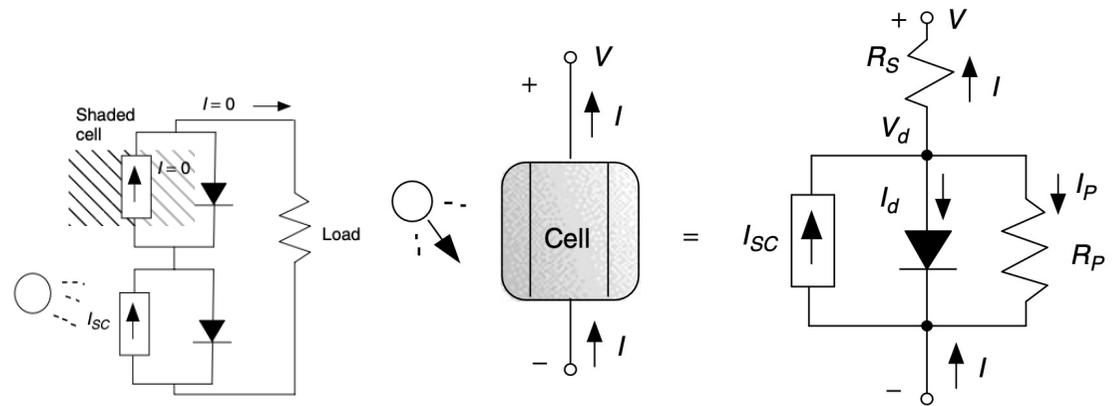


Illustration of the effects.
More reasonable: $R_p \approx 6$, $R_s \approx 0.005$

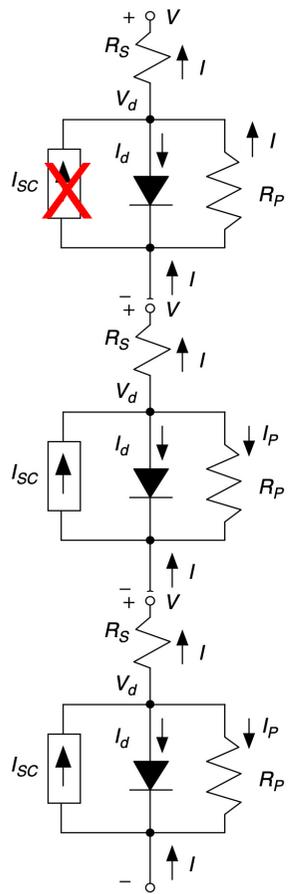An Example of shaded panels, a street light pole



Shading - One shaded cell

- Voltage from one module with a shaded cell

- n-1 cells are active

$$V_{SH} = V_{n-1} - I(R_P + R_S)$$

- Rewritten to expression in normal voltage V

$$V_{SH} = \left(\frac{n-1}{n}\right)V - I(R_P + R_S)$$


- Voltage loss in the module

$$\Delta V = V - V_{SH} = V - \left(1 - \frac{1}{n}\right)V + I(R_P + R_S)$$

$$\Delta V = \frac{V}{n} + I(R_P + R_S)$$


- R_P is much greater than R_S

$$\Delta V \cong \frac{V}{n} + IR_P$$

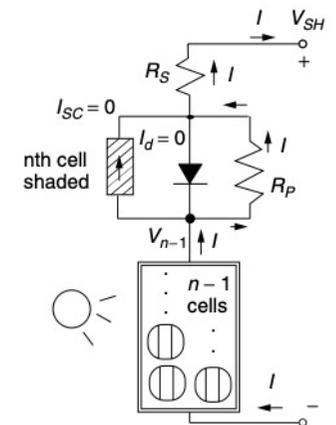

Tool to counteract the shading losses


Bypass diodes

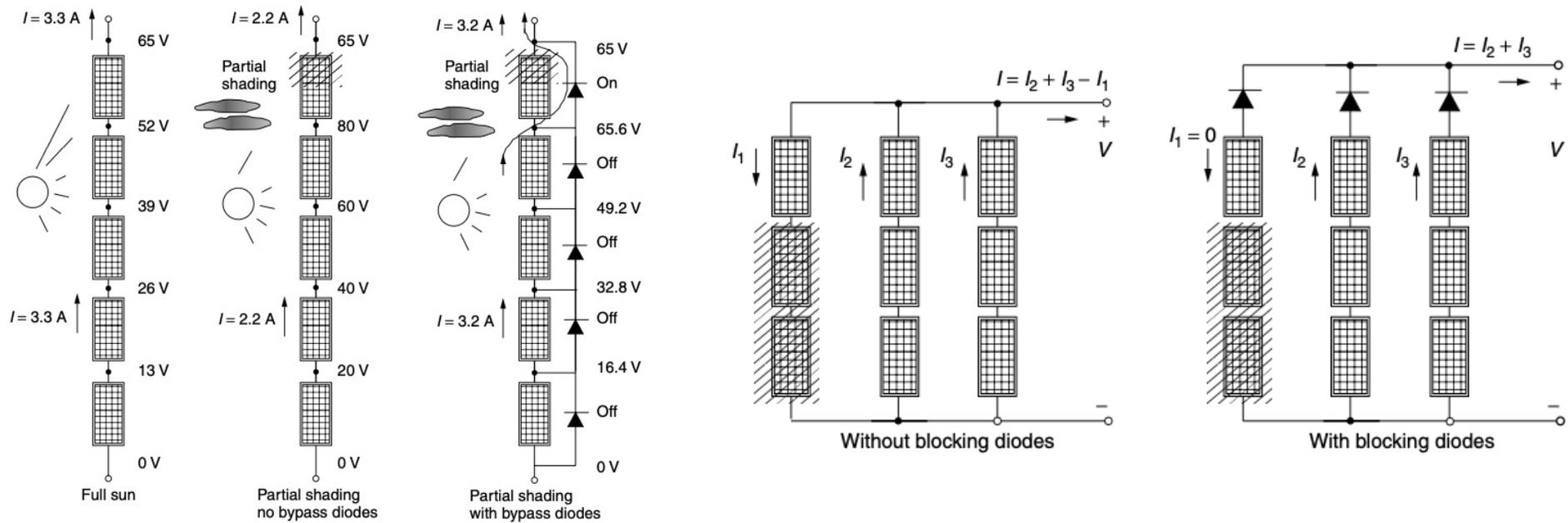

PV-module modelling

PV-module with N cells with equal solar radiation defined by
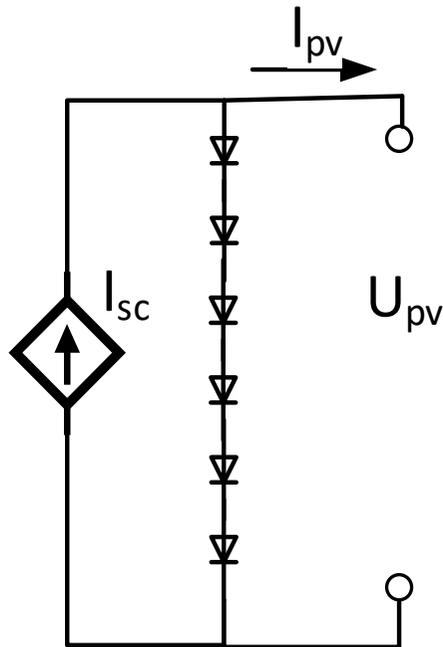
$$I_{pv} = I_{sc} - I_s \left(e^{\frac{V_{pv}}{N \cdot m \cdot V_T}} - 1 \right)$$



Open circuit conditions: $\begin{cases} I_{pv} = 0 \\ V_{pv} = V_{oc} \end{cases}$

I_s : a diode parameter, typically μA , can be calculated as

$$I_s = \frac{I_{sc}}{e^{\frac{V_{oc}}{N \cdot m \cdot V_T}} - 1}$$

IV-characteristics vs Irradiance

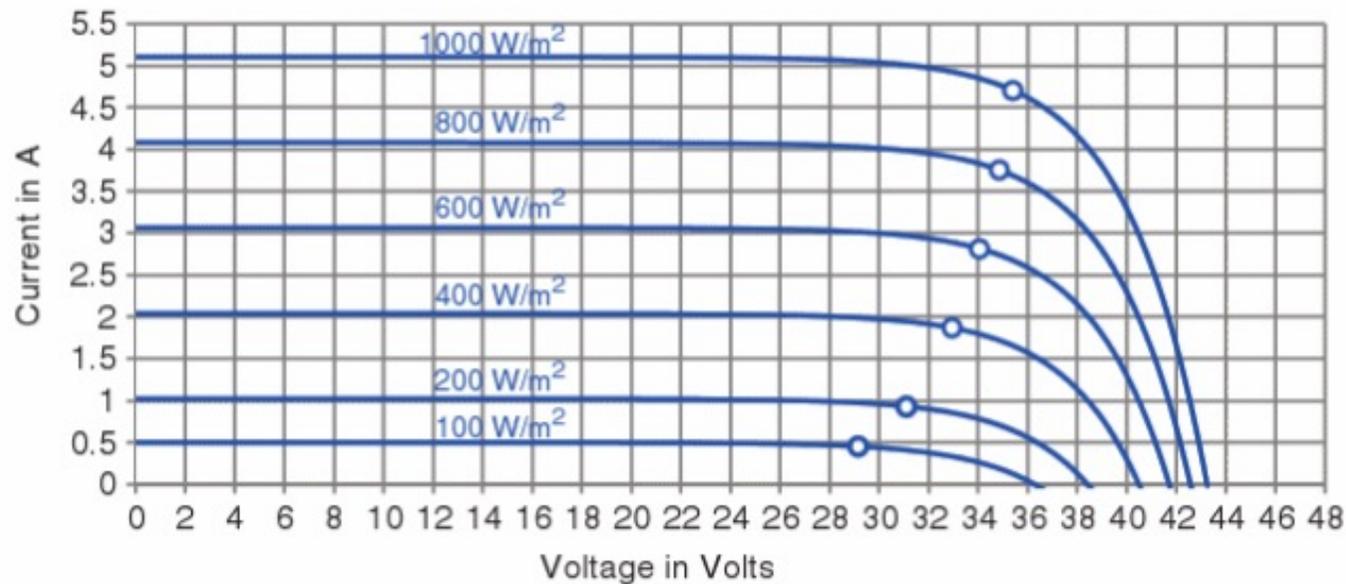


Figure 6.13 Characteristic curve of the SW-165 module at various irradiances and constant module temperature of 25 °C (Spectrum: AM 1.5)

Solar World SW-165 W,
1.6x0.8 m, Monocrystalline, 72 cells
 $V_{mp} = 35.3 \text{ V}$, $I_{mp} = 4.68 \text{ A}$,
 $V_{oc} = 43.2 \text{ V}$, $I_{sc} = 5.1 \text{ A}$

Paralleling PV-cells

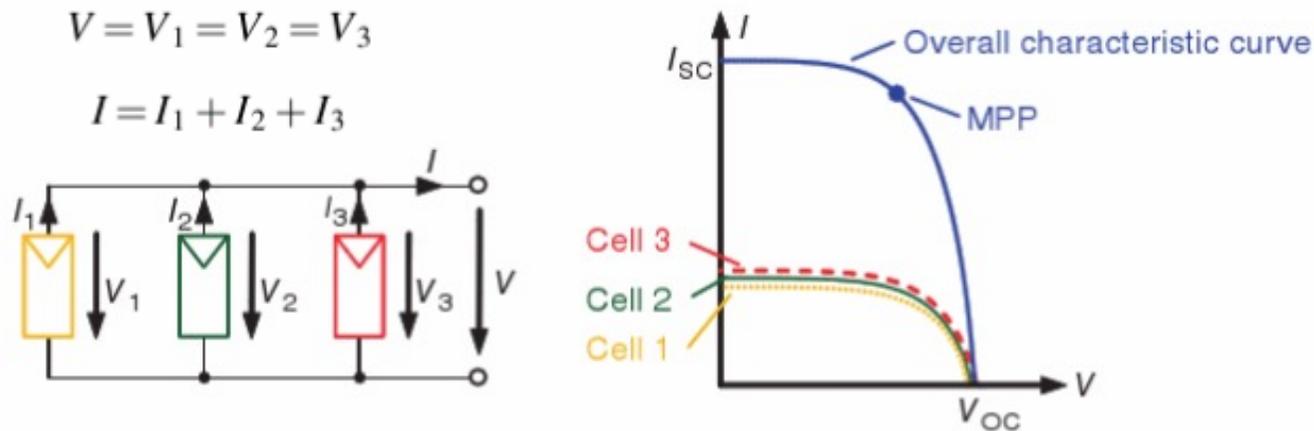


Figure 6.2 Parallel connection of solar cells: The voltage is the same in all cells while the currents add up

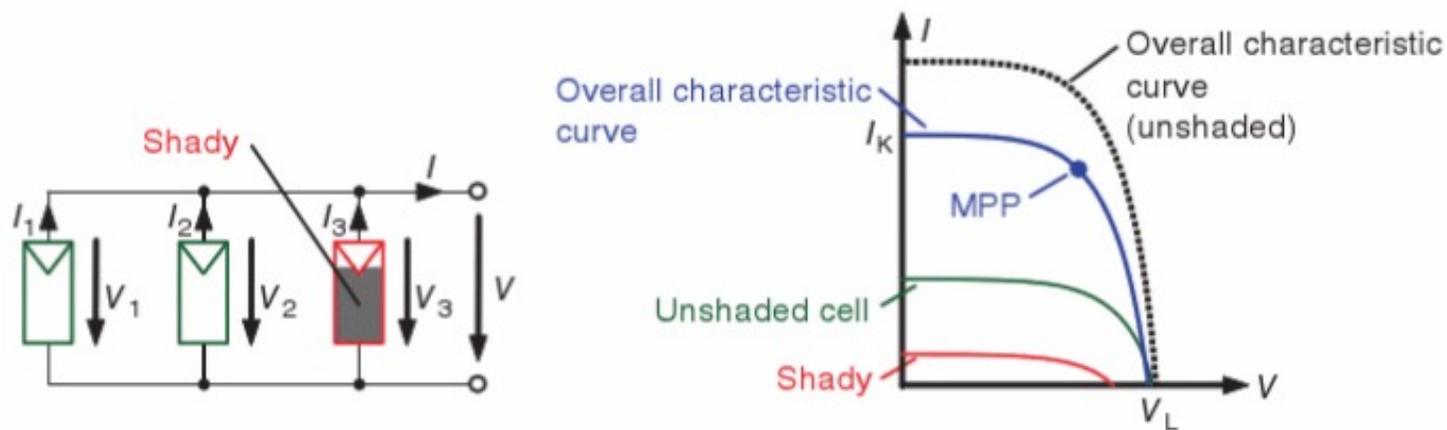


Figure 6.3 Shading one of the three cells: The current of the overall characteristic curve decays by the same amount as the current of Shady

Series connection



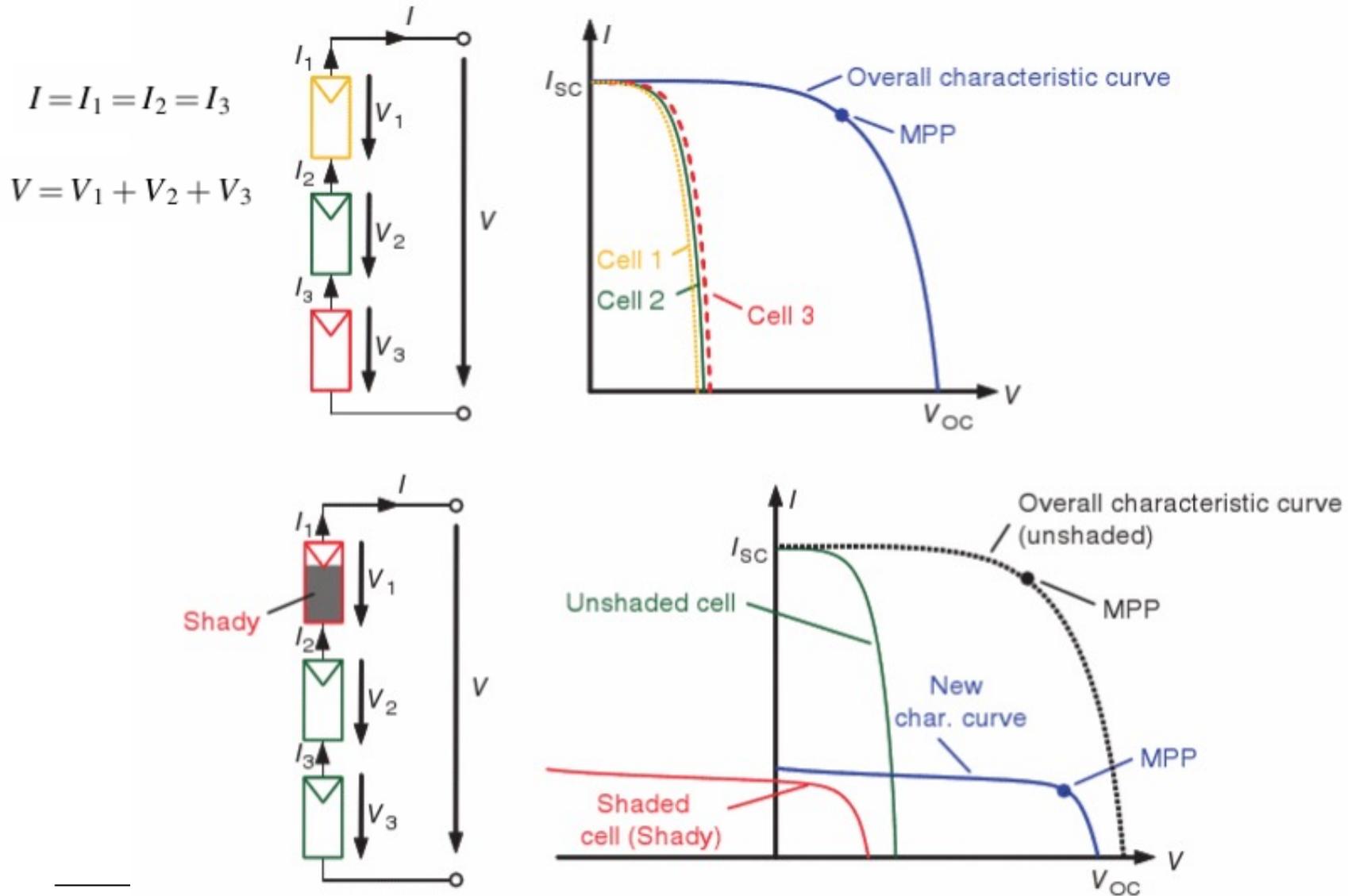


Figure 6.5 Partial shading of a cell with series connection: As Shady acts as the bottleneck, the overall current sinks strongly

Series connection. Shading

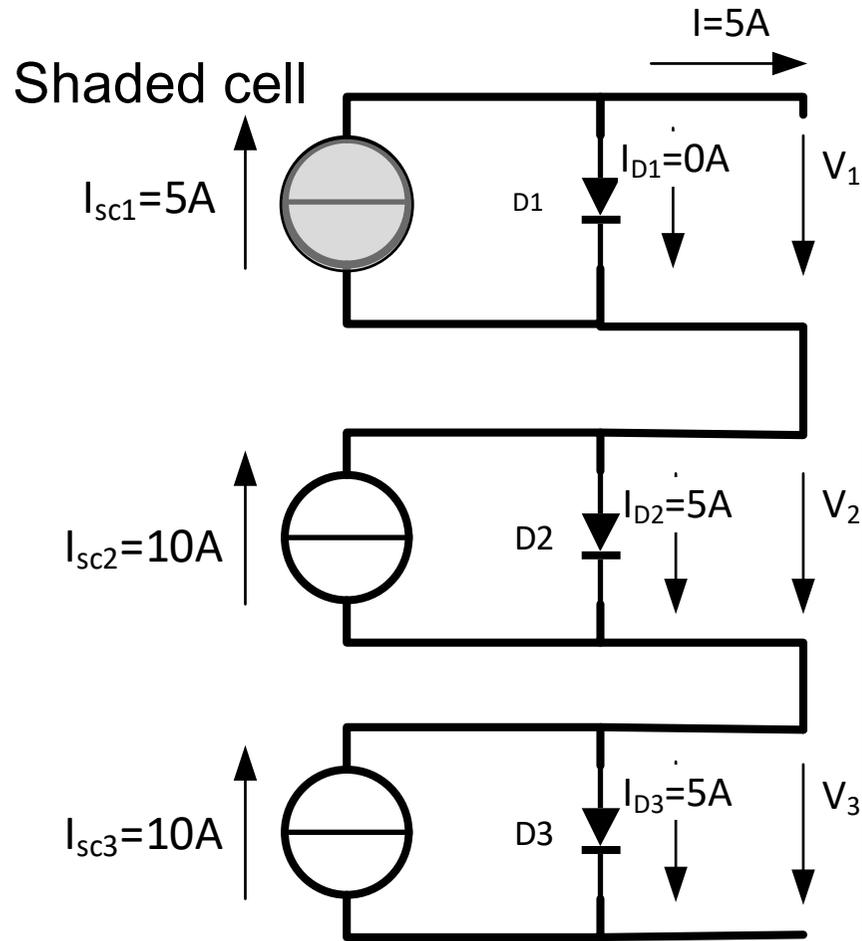

The shaded cell is limiting current

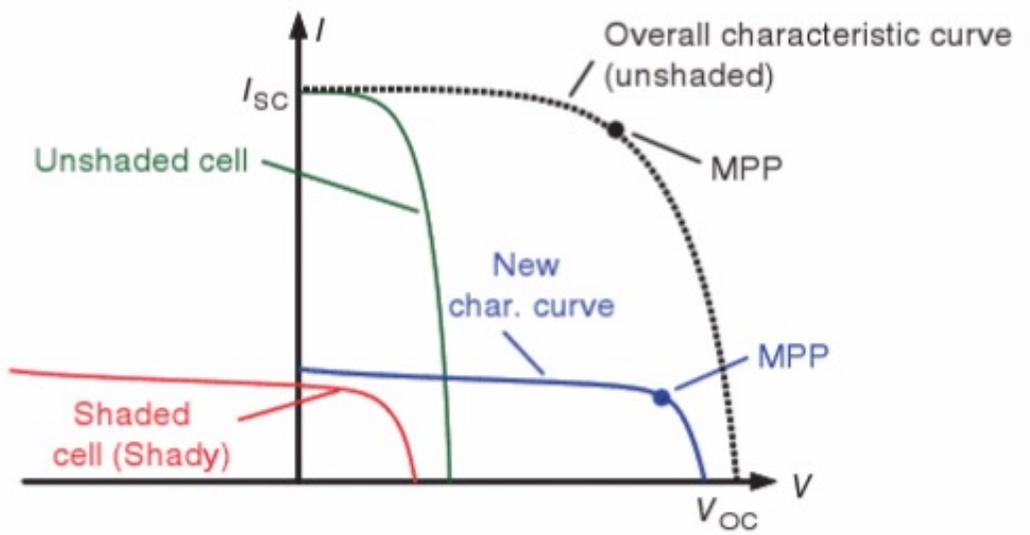

Solar module shading



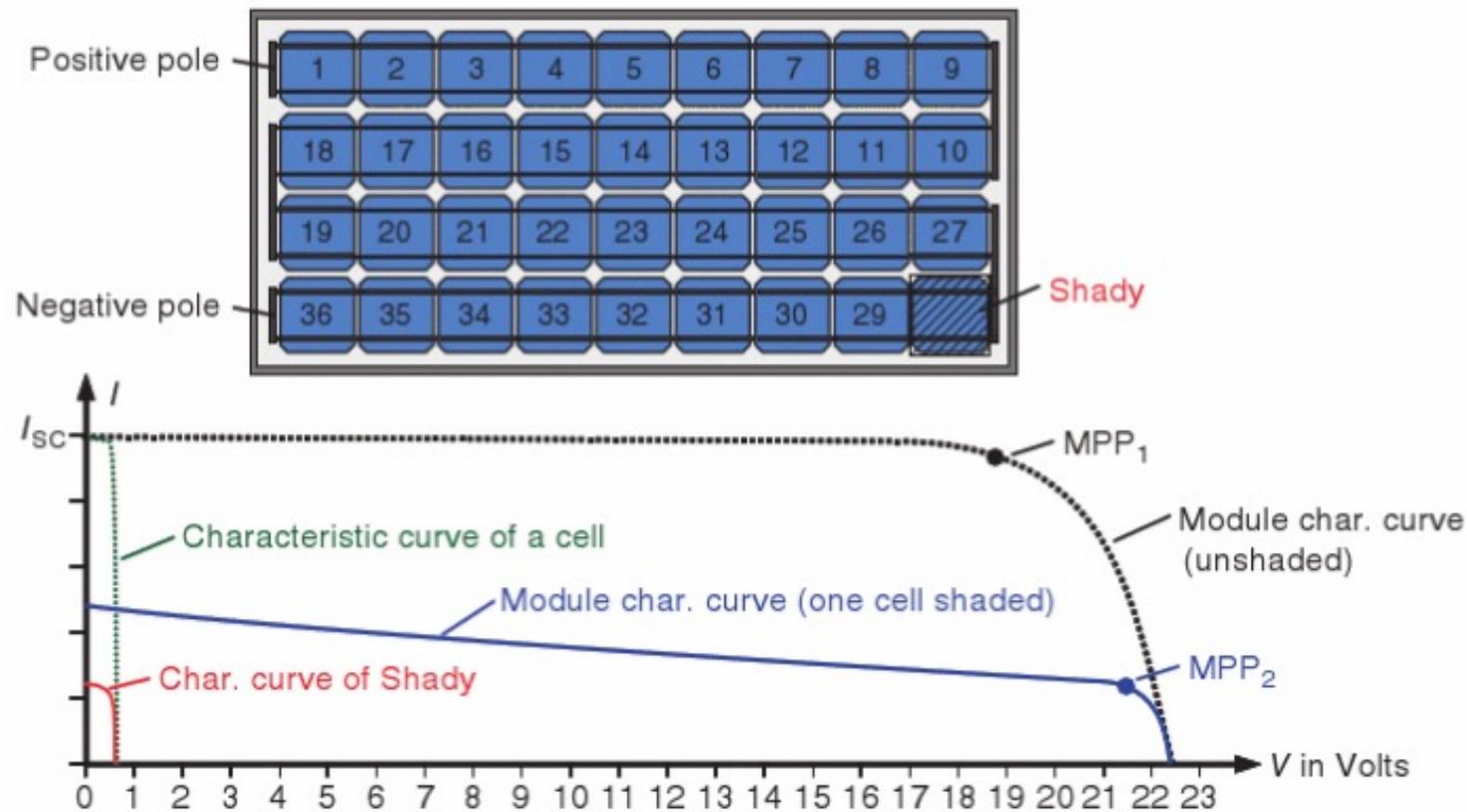


Figure 6.6 Solar module with 36 cells: The module power sinks drastically in the case of shading of a single cell

The bypass diode

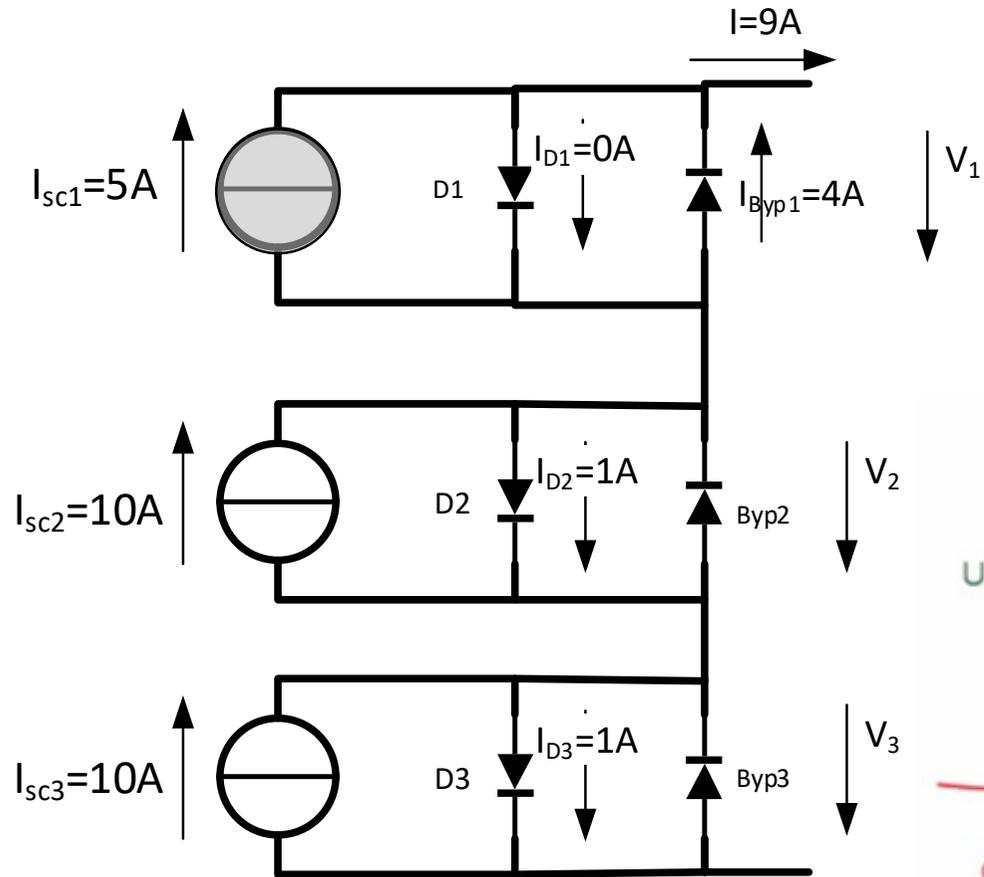

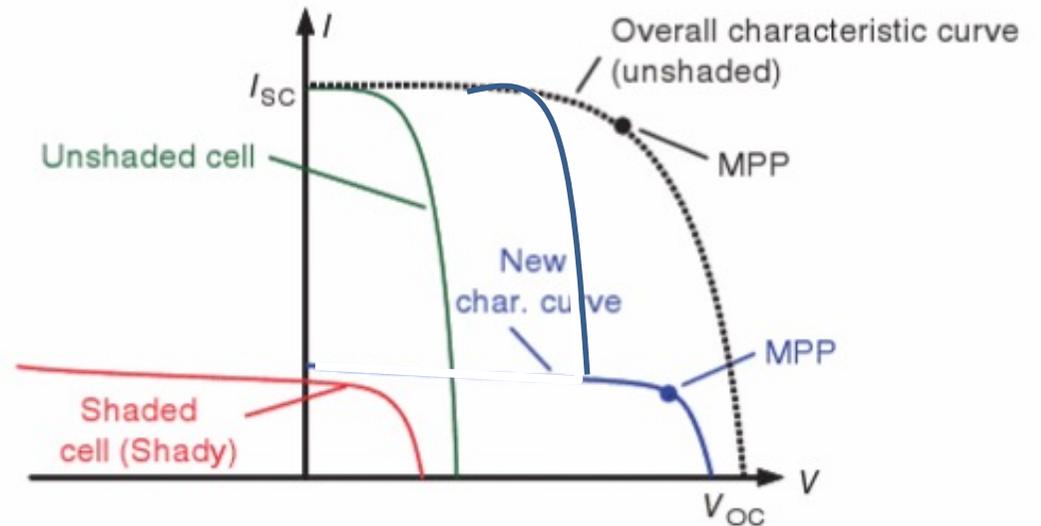Bypass diode of shaded cell carries the current deficit



Bypass diodes, ideal case


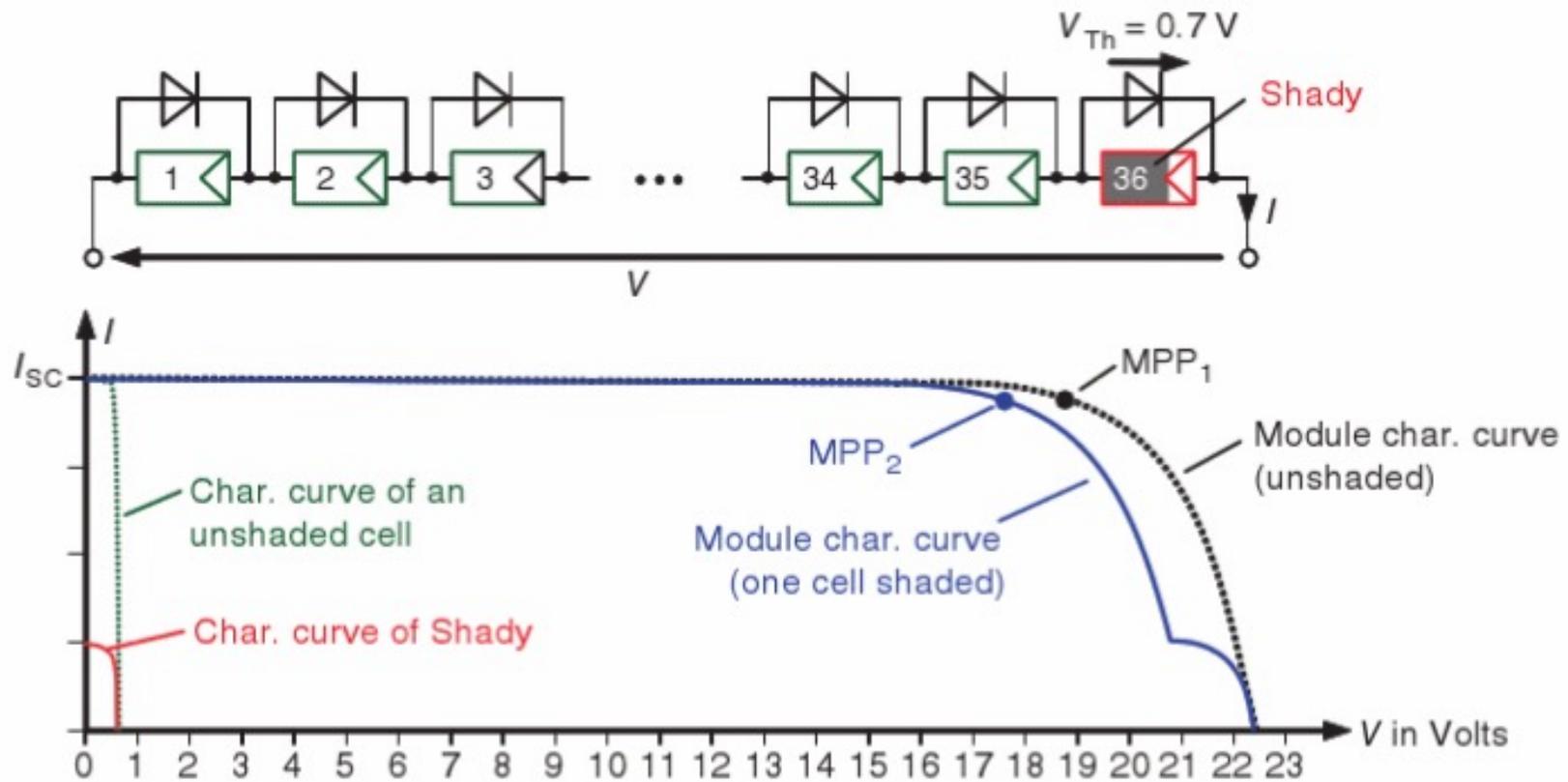


Figure 6.7 Solar module with 36 cells and bypass diode over each cell: The power loss is a minimum in the case of shading of any cell


Practical case of bypass diodes

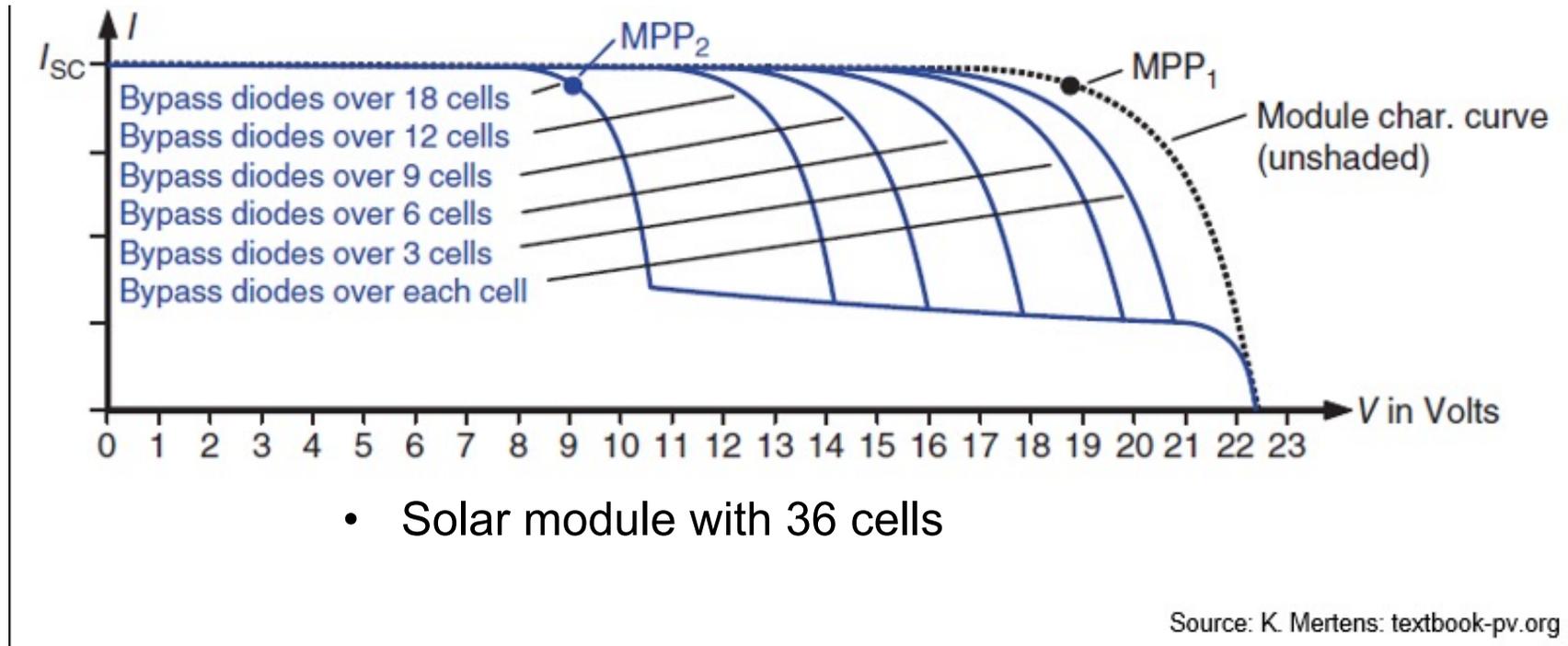

- Module design is typically using 1-3 bypass diodes
- Voltage loss from bypass diodes of shaded cells
 - Not practical to accommodate many diodes in a module housing.

The junction box

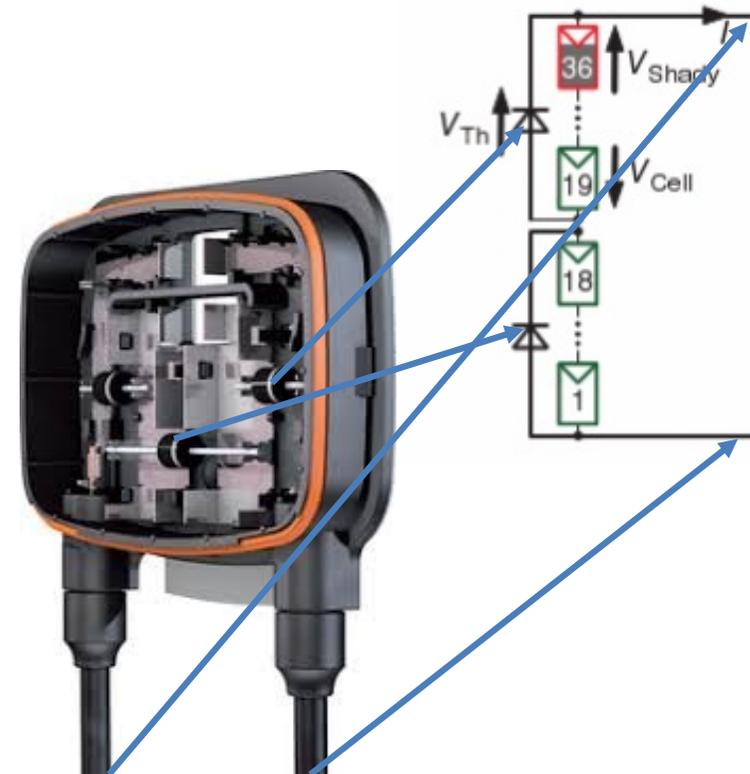Back side of the module
External connections
Bypass diodes



PV-cell characteristics

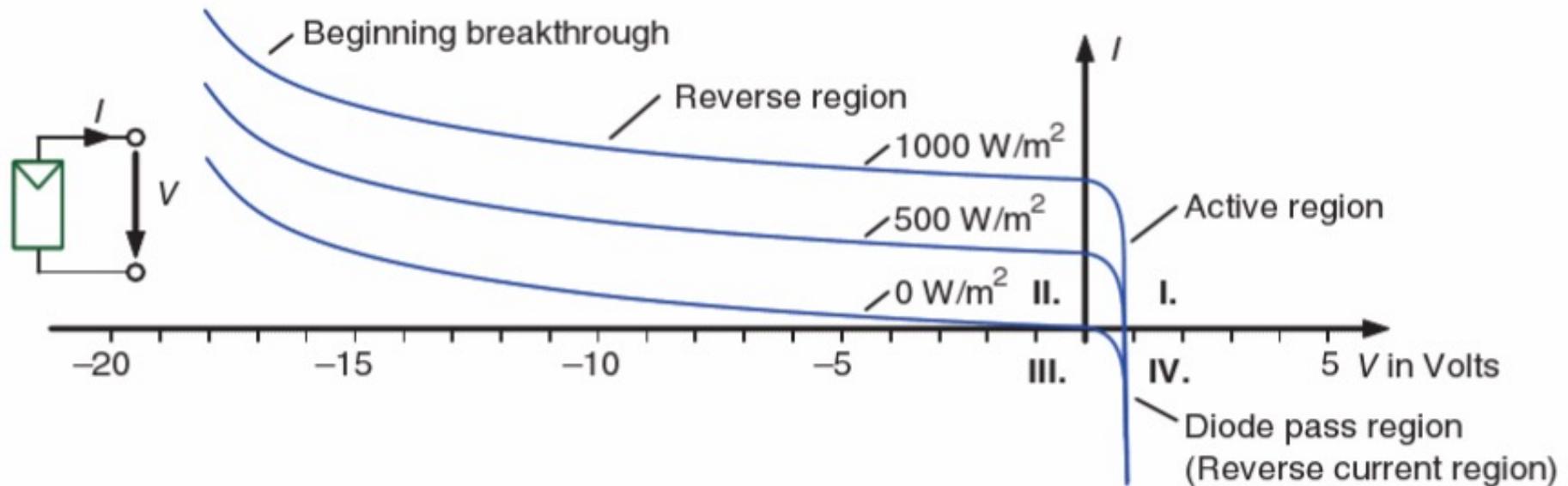


Figure 6.1 Solar cell characteristic curves in all quadrants in the generator reference-arrow system

Beginning breakthrough at high negative voltages

Critical hot spot

Module with 36 cells, shaded cell without bypass diode

- Loaded by **reverse voltage** from other 35 cells
- Beginning break-through at high reverse voltage
- Risk of overheating
- Worse case under short circuit

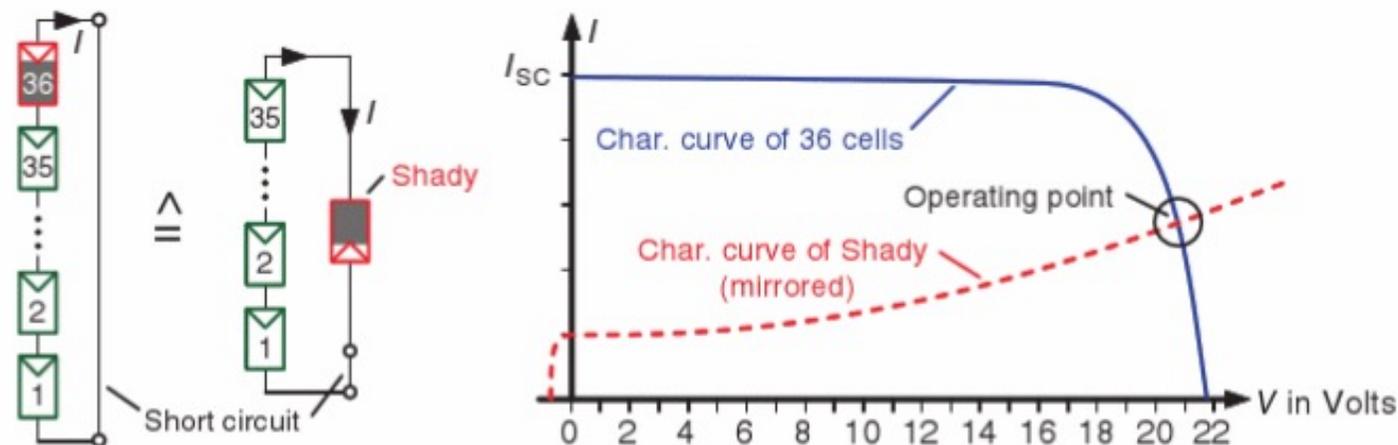


Figure 6.9 Solar module with 36 cells without bypass diodes: Shady acts as a load that is massively heated by the remaining 35 cells

Hot spots reduced with bypass diode

Bypass diode across 18 cells groups
Hot spot in shaded cell reduced to 50%

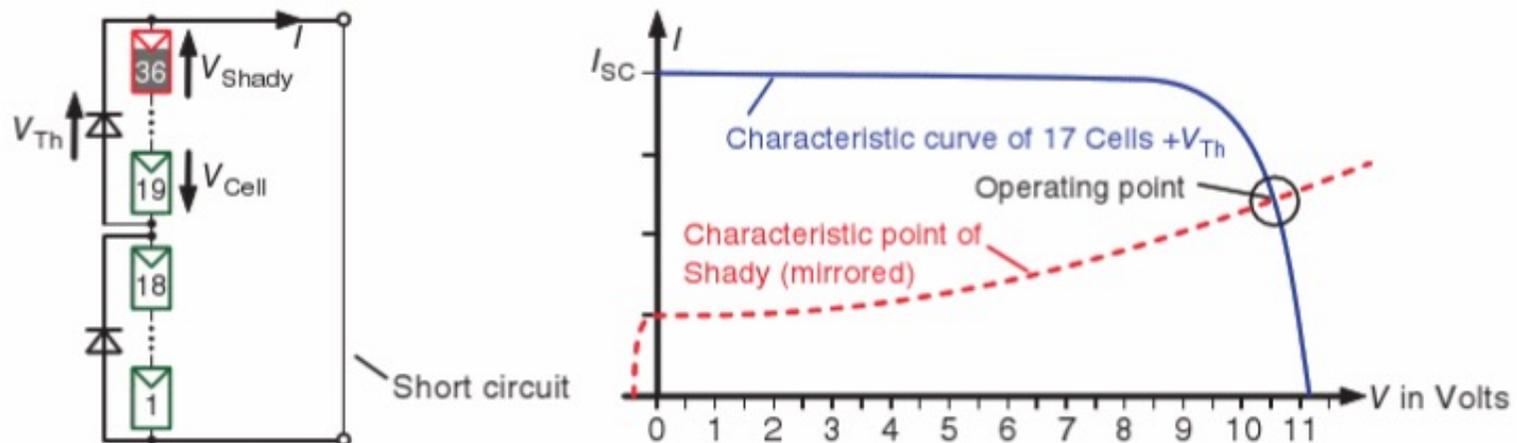


Figure 6.10 Solar module with 36 cells and two bypass diodes: The voltage at Shady clearly sinks compared with Figure 6.9 so that the heating is reduced

$$V_{Shady} = (z - 1) \cdot V_{Cell} + V_{Th}$$

Where z is the number of cells under a bypass diode.

Configuration summary

- **Paralleling** principally better to combine many cells (current sources) since current is added. Very low cell voltage (0.6V) gives high current, and **high cabling losses** when paralleling
- **Series connection** efficient to achieve high voltage at low current. **The predominant solution!**
- Shading becomes a **bottleneck** for current reducing output power of also unshaded cells.
- Shaded cells, can be overloaded by unshaded cells. **Hotspot.**
- **Bypass diodes** used to mitigate consequences of shading for series connection.

Temperature dependency



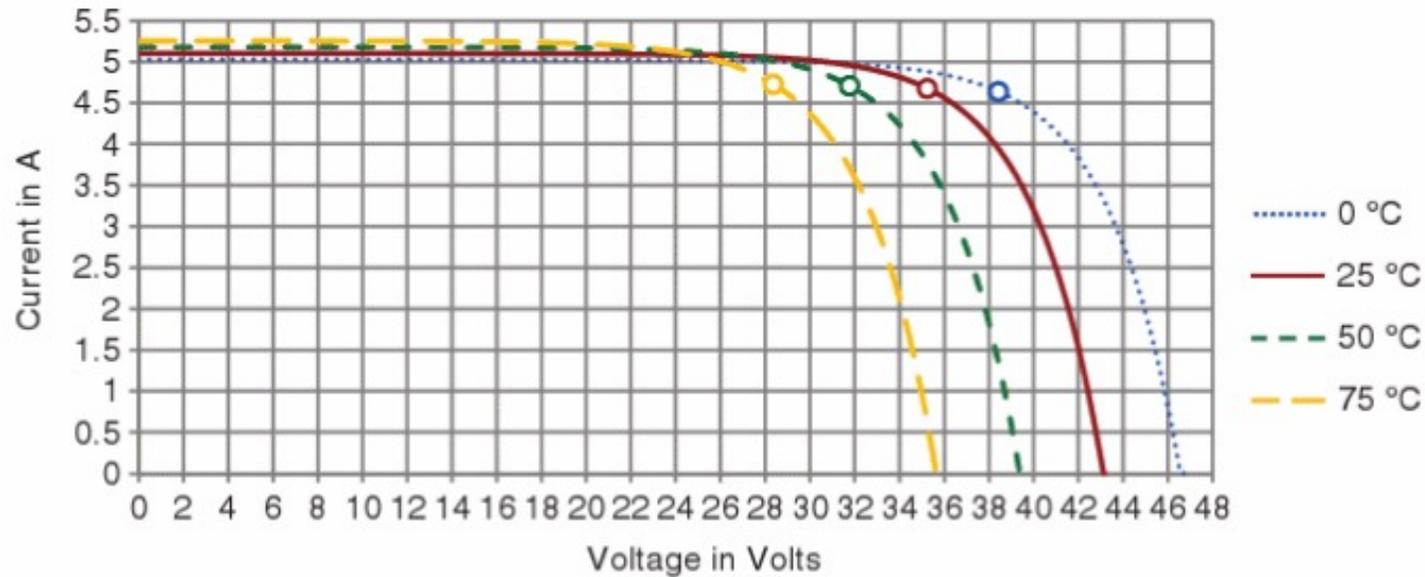


Figure 6.14 Characteristic curve of the SW-165 module from Solarworld at various module temperatures (Irradiance: 1000 W/m^2 , spectrum: AM 1.5)

Temperature dependency

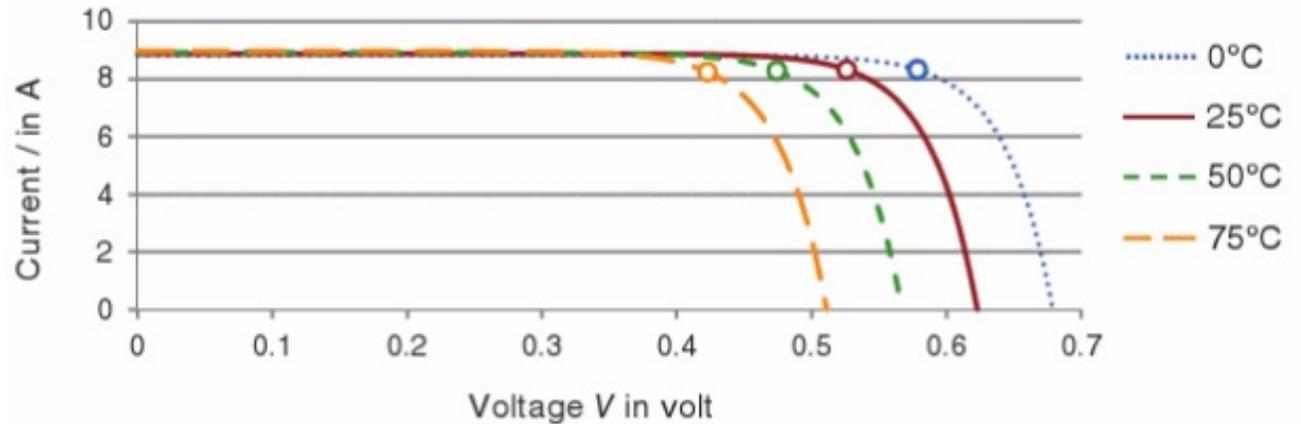
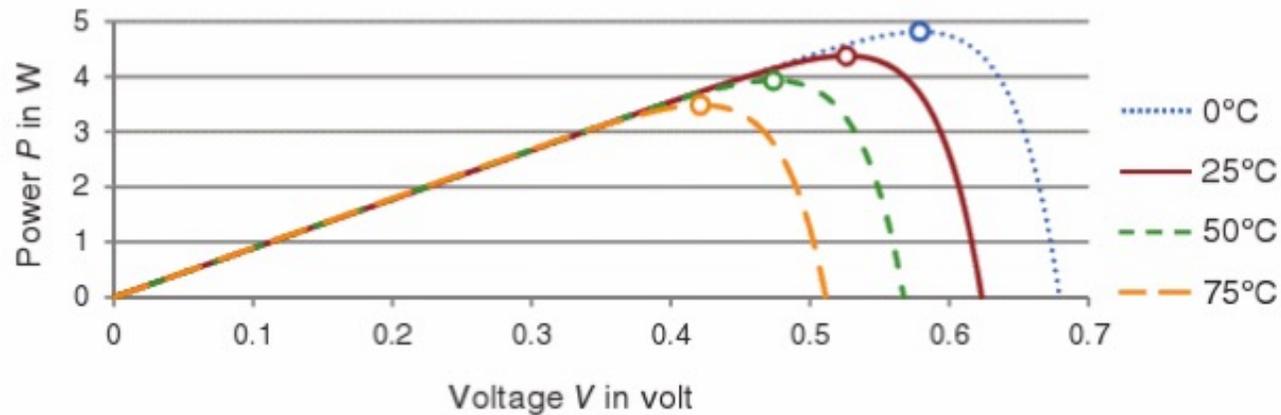
$$\frac{\Delta V_{OC}}{\Delta \vartheta} = -2.3 \text{ mV/K}$$



$$TC(P_{MPP}) = \frac{\Delta P_{MPP}}{\Delta \vartheta \cdot P_{MPP}} = -0.4 \dots 0.5 \% / K$$

Monocrystalline 156x156mm Bosch
solar cell M 3BB

Typical Si-Solar cell

Cell operating temperature

Nominal Operating Cell Temperature, NOCT


$$NOCT = \vartheta_{cell} @ E = 800 \text{ W/m}^2, \vartheta_A = 20^\circ\text{C}$$

- Irradiance: $E = E_{NOCT} = 800 \text{ W/m}^2$
- Ambient temperature: $\vartheta_A = 20^\circ\text{C}$
- Wind speed: 1 m/s

$$\vartheta_{cell} = \vartheta_A + (NOCT - 20) \frac{E}{E_{NOCT}}$$

$$\frac{\vartheta_{cell} - \vartheta_A}{NOCT - 20} = \frac{E}{E_{NOCT}}$$

Standard Test Conditions (STC)

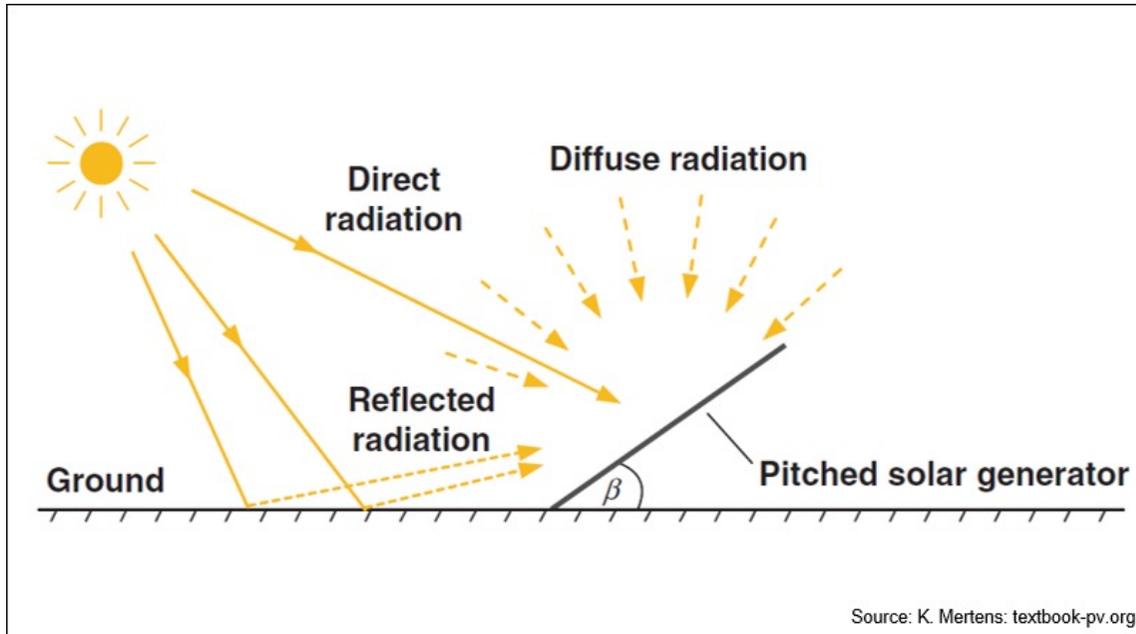

$$E_G = E_{\text{Direct}} + E_{\text{Diffuse}}$$

- $E_G = E_{STC} = E_{\text{Direct}}(AM1.5) + E_{\text{Diffuse}} = 1000 \text{ W/m}^2$
- Module temp, $\vartheta_{\text{cell}} = 25^\circ\text{C}$
- $AM = 1.5$

PV module

320 W at STC

1.6 m²

5kW = 15.6 modules

Total 25 m²

Elektriska egenskaper(STC 1000W/m², 25°C, AM1.5)


Modell	PPAM-Onyxium
Max. Effekt [Pmax]	320 Wp
Öppenkretsspänning [Voc]	40,67 V
Spänning vid maxeffekt [Vmpp]	32,25 V
Kortslutningsström [Isc]	10,49 A
Ström vid maxeffekt [Impp]	9,92 A
Modulens effekttolerans	0/+3%
Verkningsgrad panel modul	19,76%

Fysiska egenskaper

Celltyp	Monokristalin
Celldimensioner	156x156mm
Celler/Dioder per modul	60
Ram	Anodiserad Aluminium
Max spänning system	1000 V
Modulvikt	19,5 kg
Moduldimensioner	1640 x 990 x 40mm
Testade väder temperaturer	-40°C to +85°C
Max belastning	550 kg/m ² framsida(snö) 245 kg/m ² bak & framsida (vind)

Termiska egenskaper

NOCT	46 °C
Spänning temperaturkoefficient	-0.24%/K
Temperatur koefficient ström	+0.032%/K
Temperatur koefficient effekt	-0,40%/K

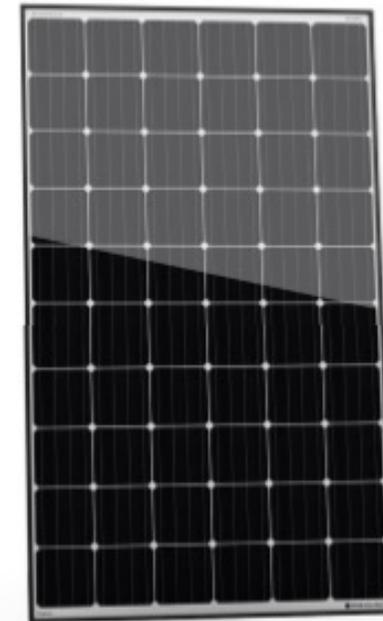

Example 6.1 Actual module power on a summer's day

The 200 W *Bosch c-Si M48-200* solar module has a NOCT temperature of 48.6 °C. What module power can be expected on a nice summer's day ($E = 1000 \text{ W/m}^2$, $\vartheta_A = 30 \text{ °C}$)?

The actual cell temperature is:

$$\vartheta_{cell} = \vartheta_A + (NOCT - 20) \frac{E}{E_{NOCT}} = 30 + (48,6 - 20) \frac{1000}{800} = 65,75 \text{ °C}$$

With the temperature coefficient $TC(P_{MPP})$ we obtain as actual power: $TC(P_{MPP}) = -0.47 \text{ \%}/K$

$$P = P_{STC} \cdot [1 + TC(P_{MPP}) \cdot (\vartheta_{Cell} - 25 \text{ °C})] = 200 \text{ W} \cdot (1 - 0.47\%/K \cdot 40.75 \text{ K}) = 161.7 \text{ W}$$

The **200 W module** thus **generates only** a power of **161.7 W**.

Reduced temperature impact


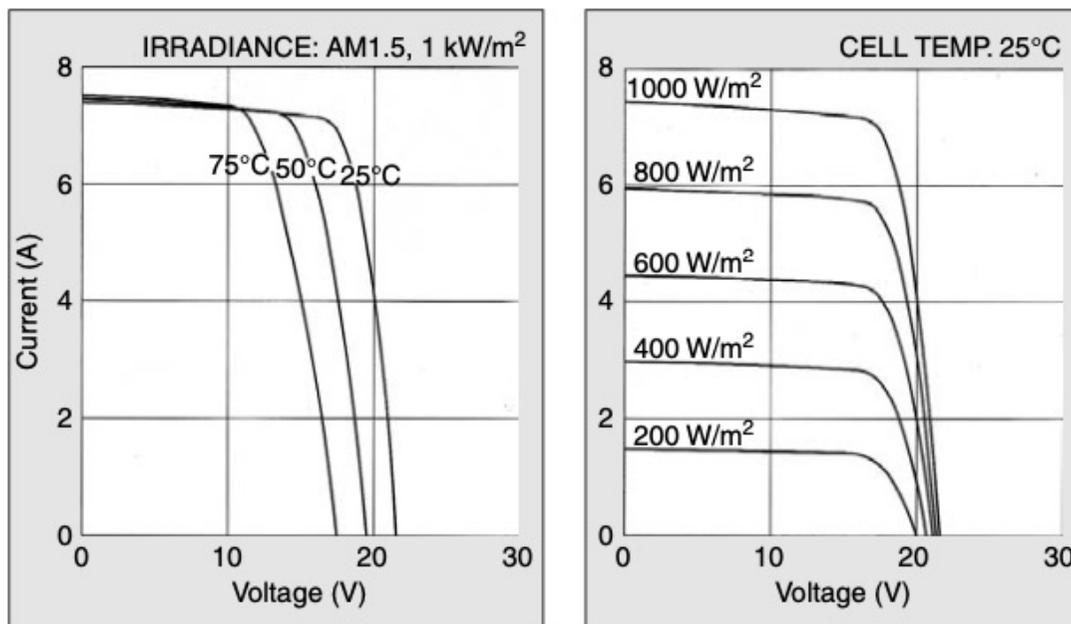


Figure 8.36 Current-voltage characteristic curves under various cell temperatures and irradiance levels for the Kyocera KC120-1 PV module.

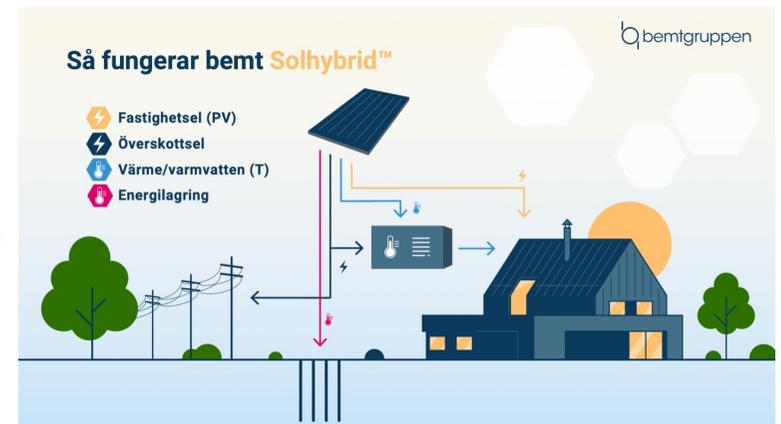- Cooling increases power, efficiency and lifetime.
- Swedish SolHybrid combines
 - Solar cell
 - Solar heating
 - Geothermal heating



Grid connection

- DC/DC conversion
- Maximum power point tracking
- Grid inverter

Solar modules and resistive load

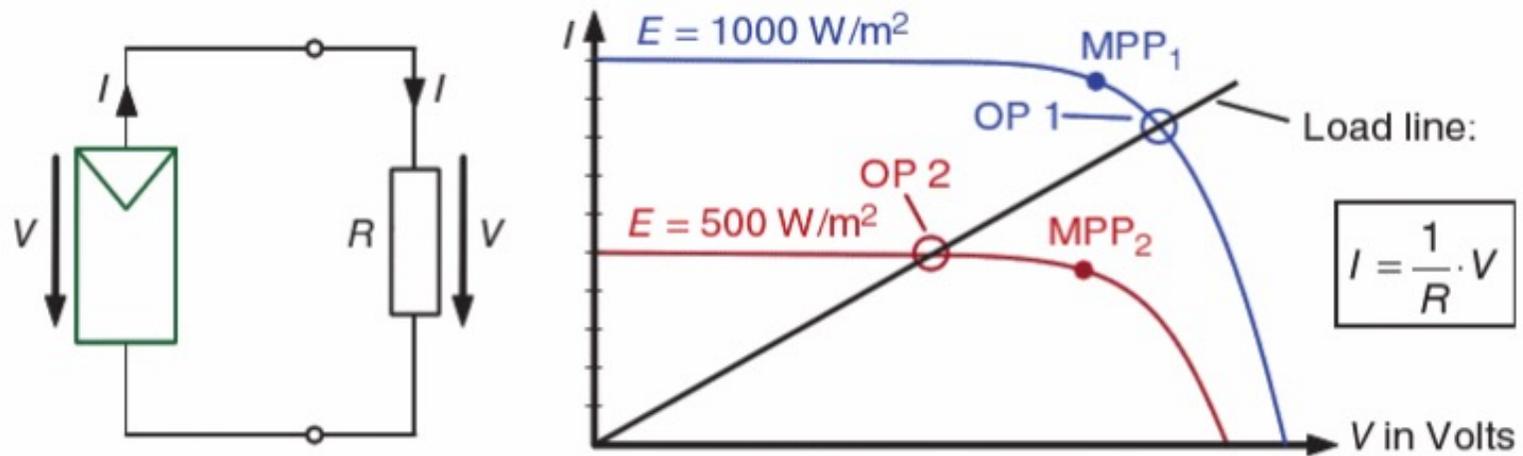


Figure 7.1 Operation of an ohmic load at a solar module: In the case of half the Sun's irradiance ($E = 500 \text{ W/m}^2$), the operating point (OP_2) is far away from MPP_2

Solar modules and DC/DC conv


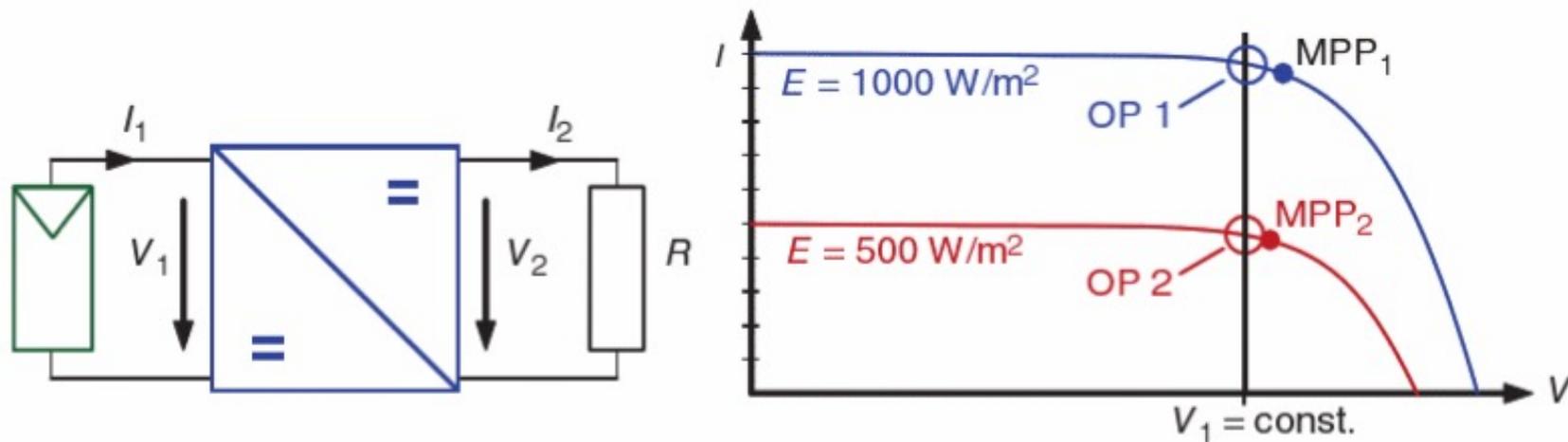
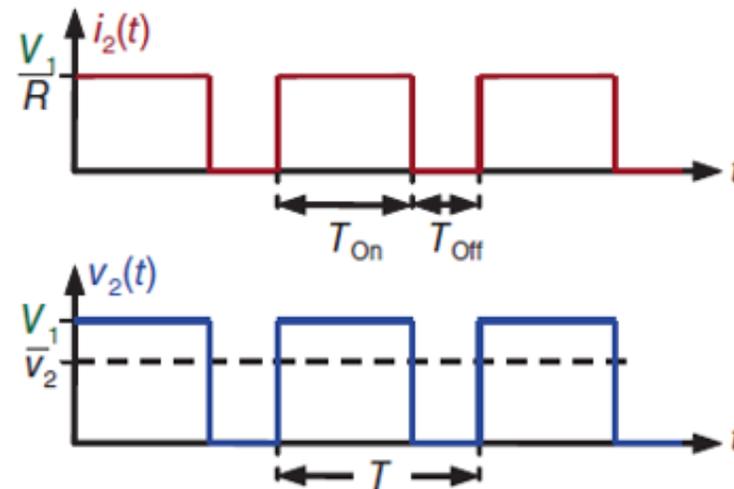


Figure 7.2 Application of a DC/DC converter: The voltage at the solar generator can be selected independently of that at the load; for example, it can be left constant



DC/DC step-down(buck) converter
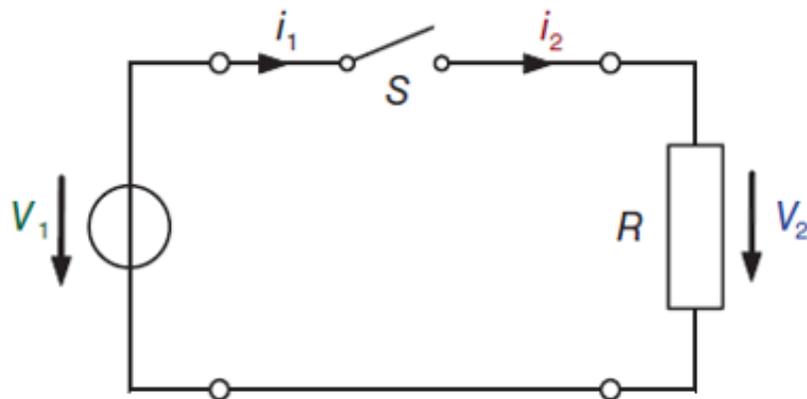
$$\frac{V_2}{V_1} = \frac{T_{on}}{T} = D, 0 < D(\text{Duty cycle}) < 1$$



Source: K. Mertens: textbook-pv.org


DC/DC step-down(buck) converter

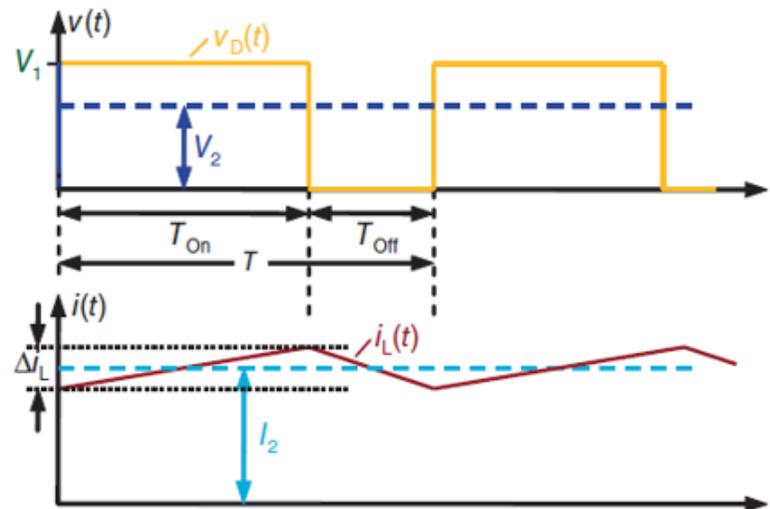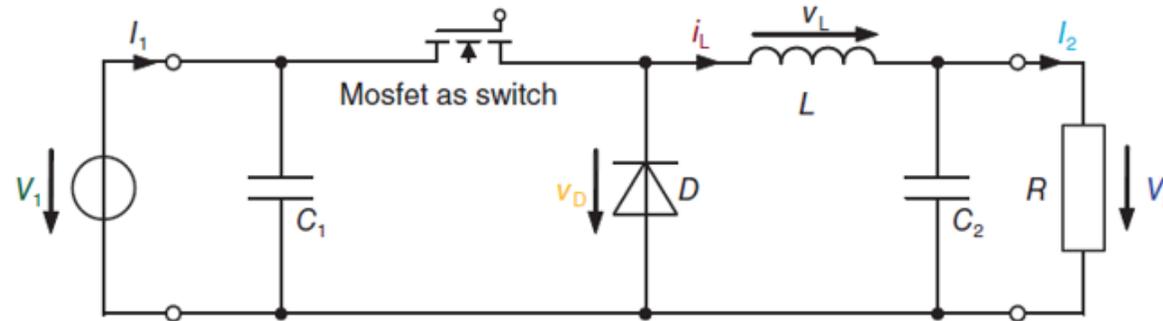

$$\frac{V_2}{V_1} = \frac{T_{on}}{T} = D$$



Source: K. Mertens: textbook-pv.org

DC/DC step-up(boost) converter

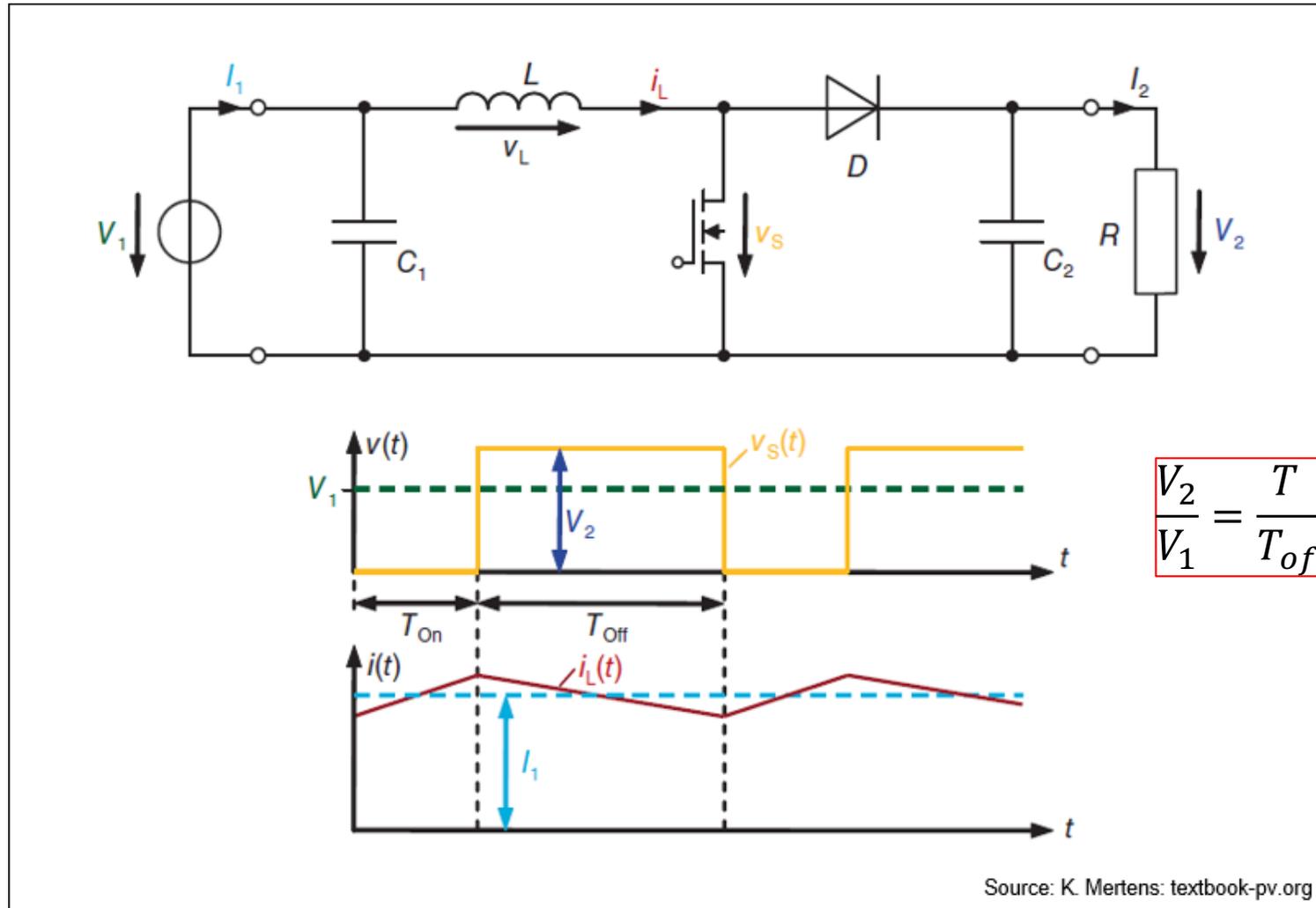


MPPT, Maximum Power Point Tracking

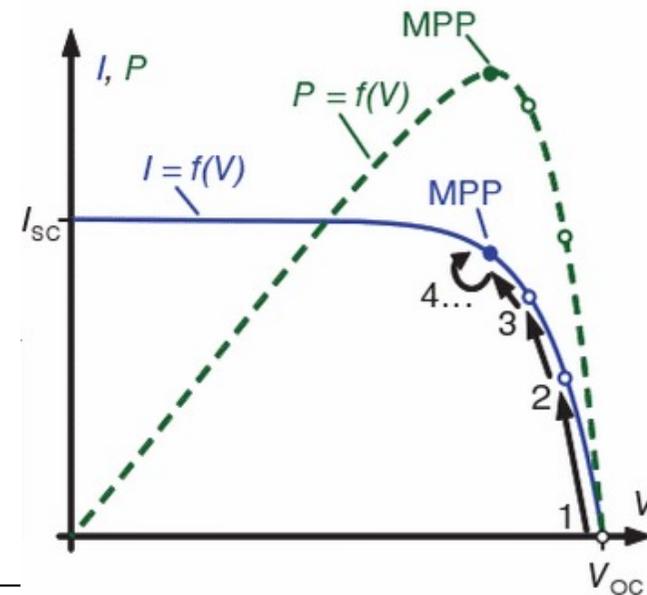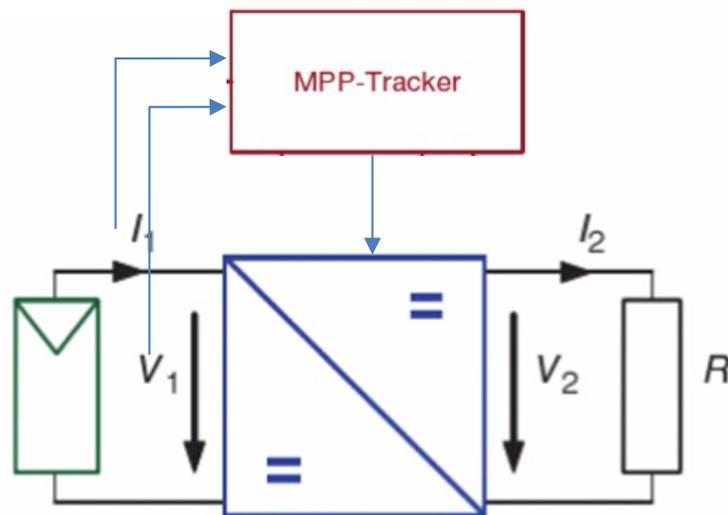- DC/DC converter to allow different pv- and load voltage
- PV-voltage is optimized to reach MPP




MPPT Perturb & Observe (PandO)

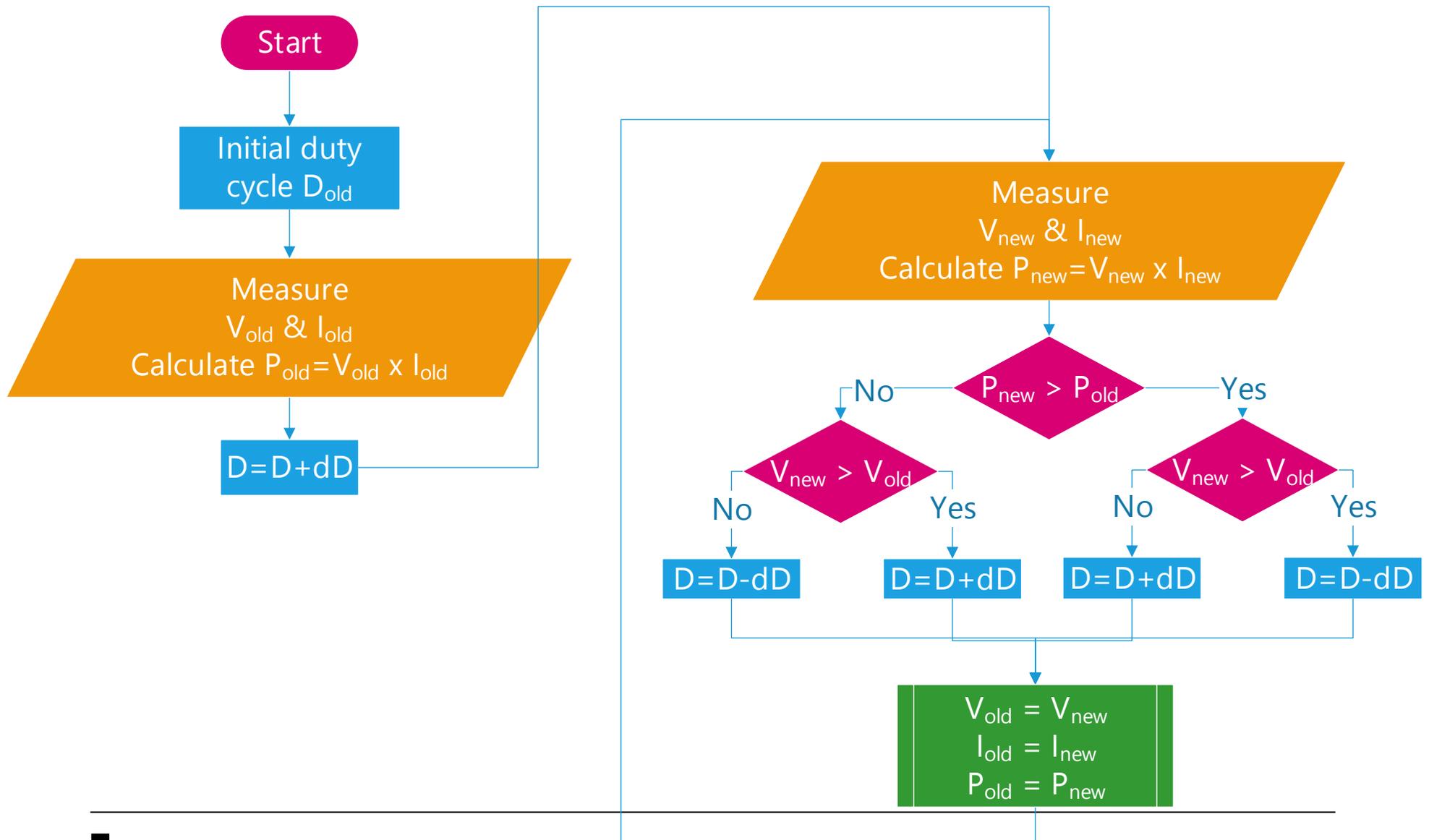

MPPT for partial shading

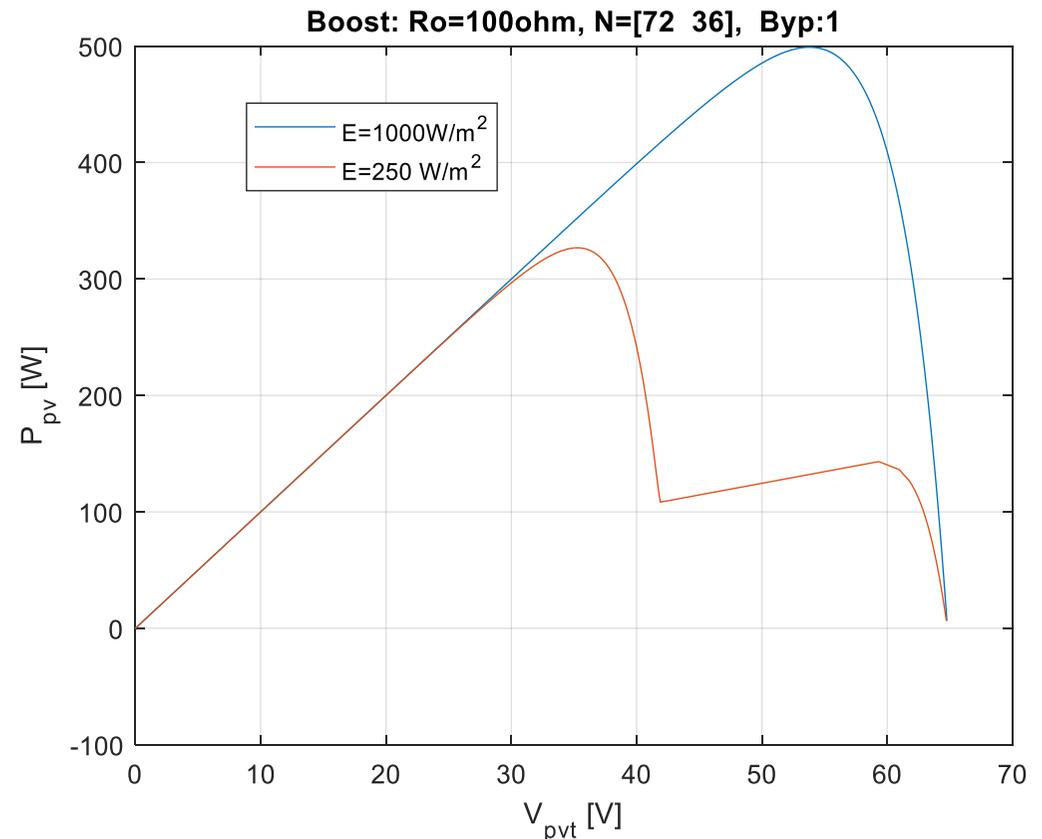- Partial shading may give multiple local MPPs
- PandO might not find the MPP
- Global scan over larger range required



Parallel strings for high power


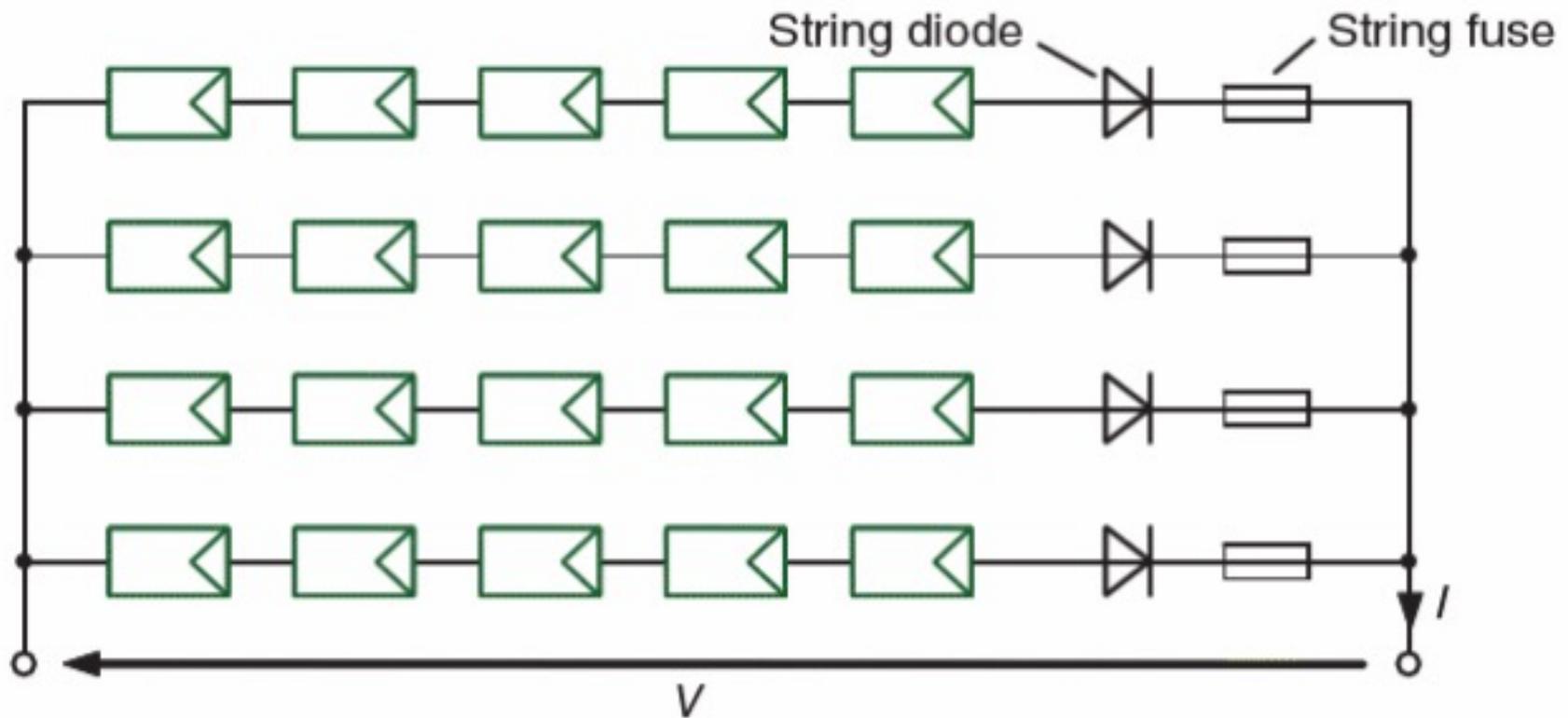


Figure 6.17 Structure of a solar generator with several strings

Grid connection

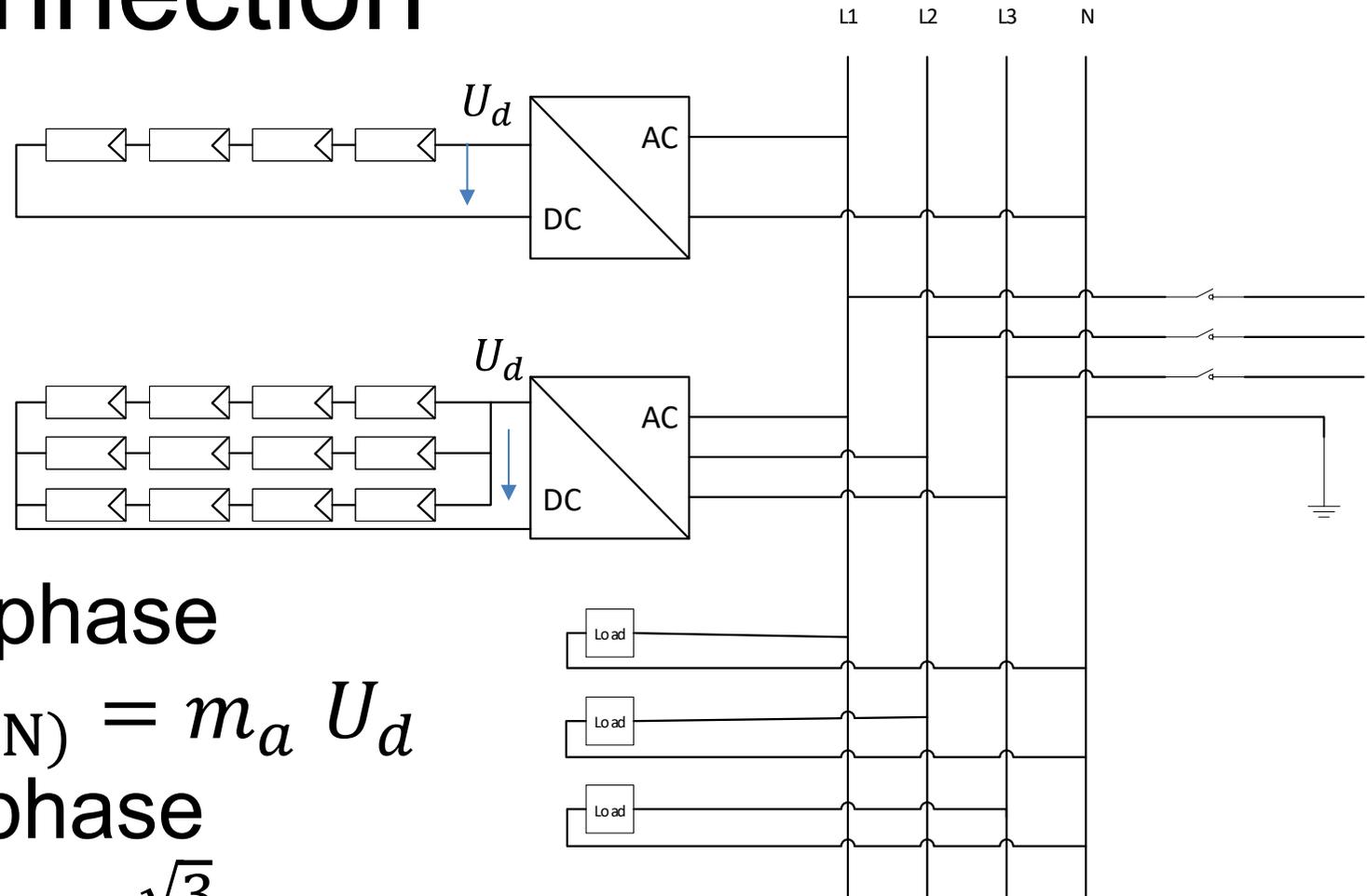

- Single phase




$$\hat{U}_{ac(L1-N)} = m_a U_d$$

- Three phase

$$\hat{U}_{ac(L-L)} = \frac{\sqrt{3}}{2} m_a U_d$$

$$m_a < 1$$


Grid inverter configurations

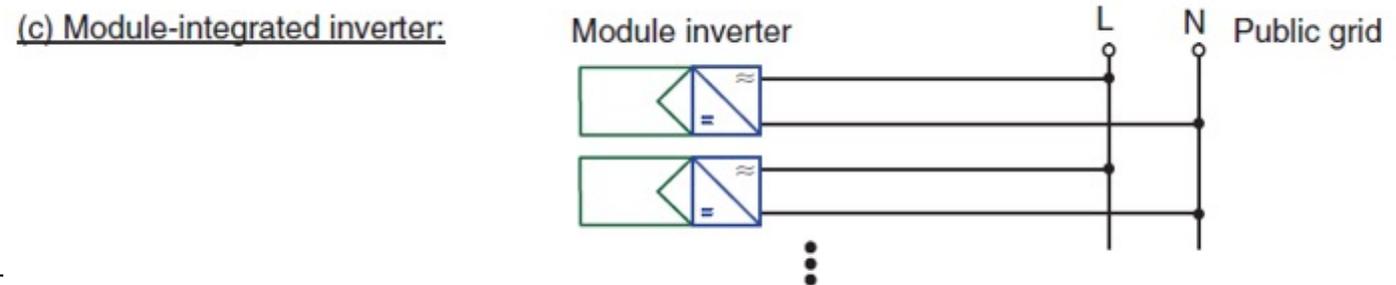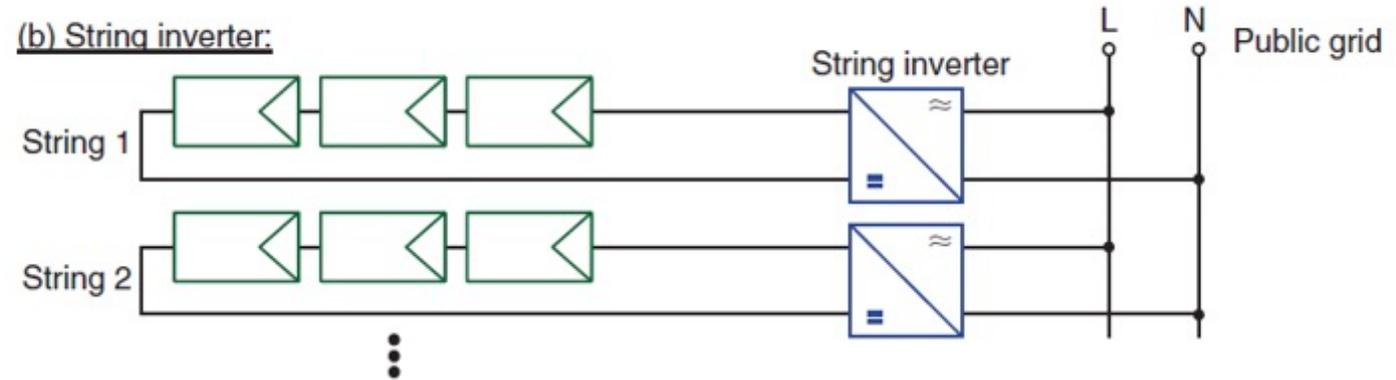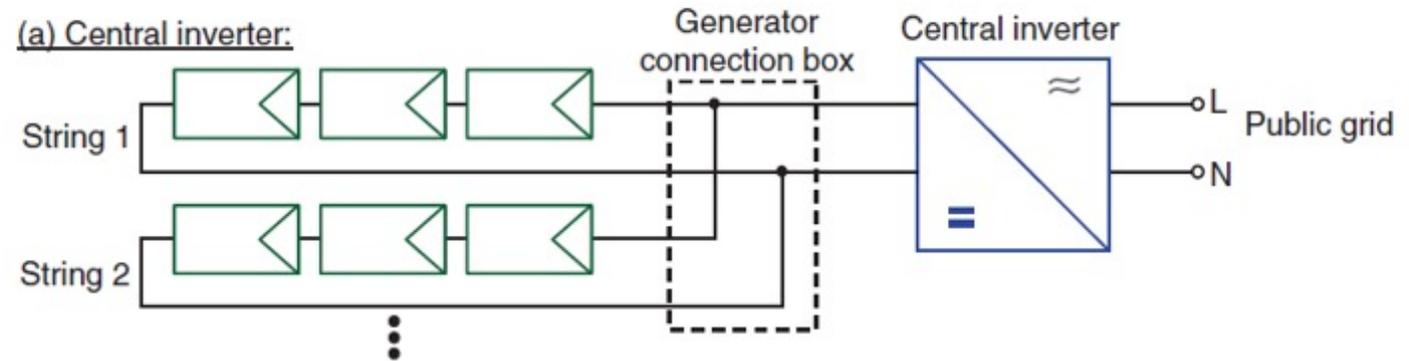

Grid inverter tasks

- Converting direct current to alternating current
- DC voltage at similar amplitude as the ac-voltage
 - - else, DC/DC boost converter required
- MPP tracking
 - Fixed ac-side voltage amplitude
 - Variable dc-side voltage
- Synchronizing infeed to the grid voltage
- Detecting stand-alone operation



Typical small PV-system

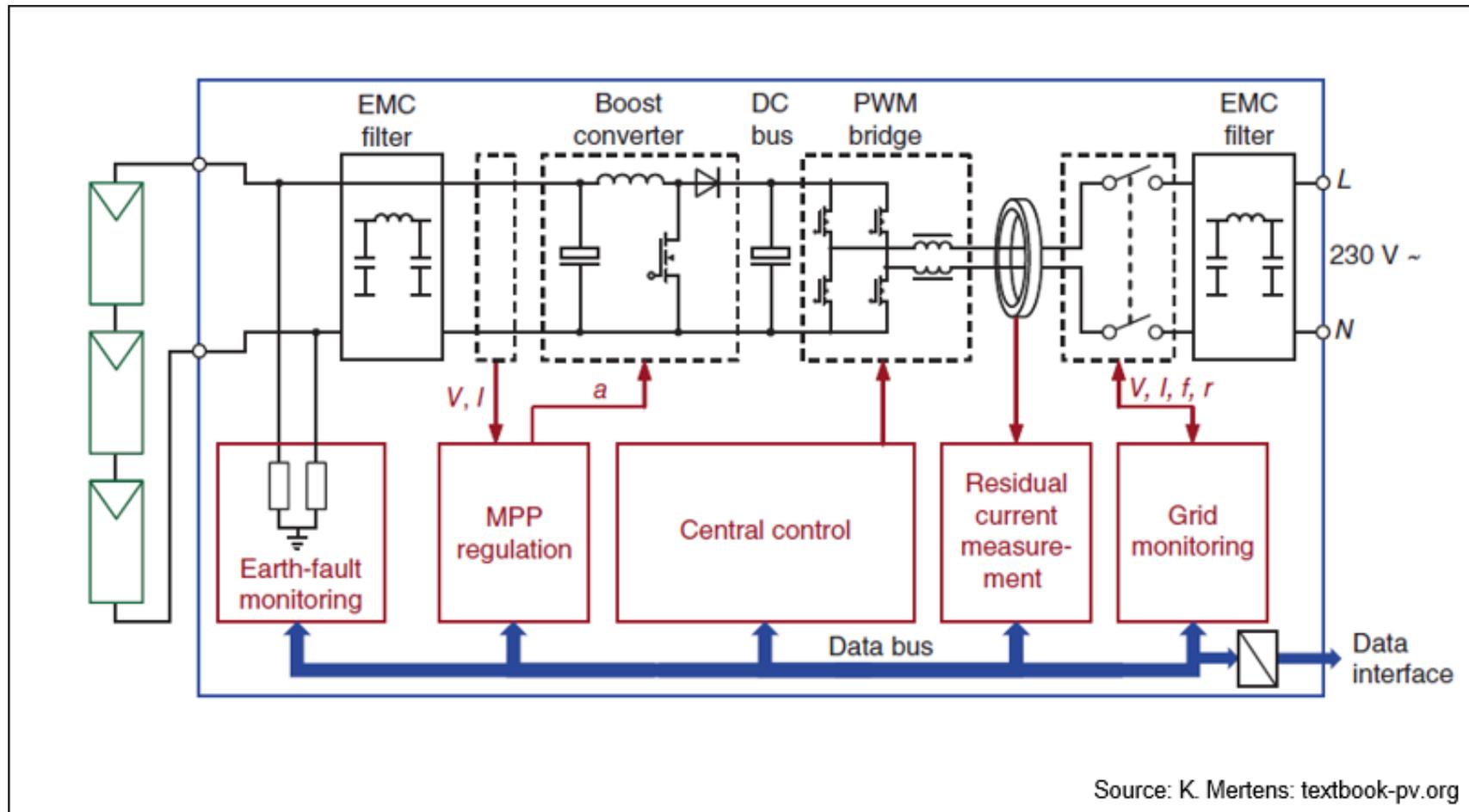


Lab1 introduction

- PV-module emulator
- Partial shading
- DC/DC Boost MPPT converter

PV-emulator

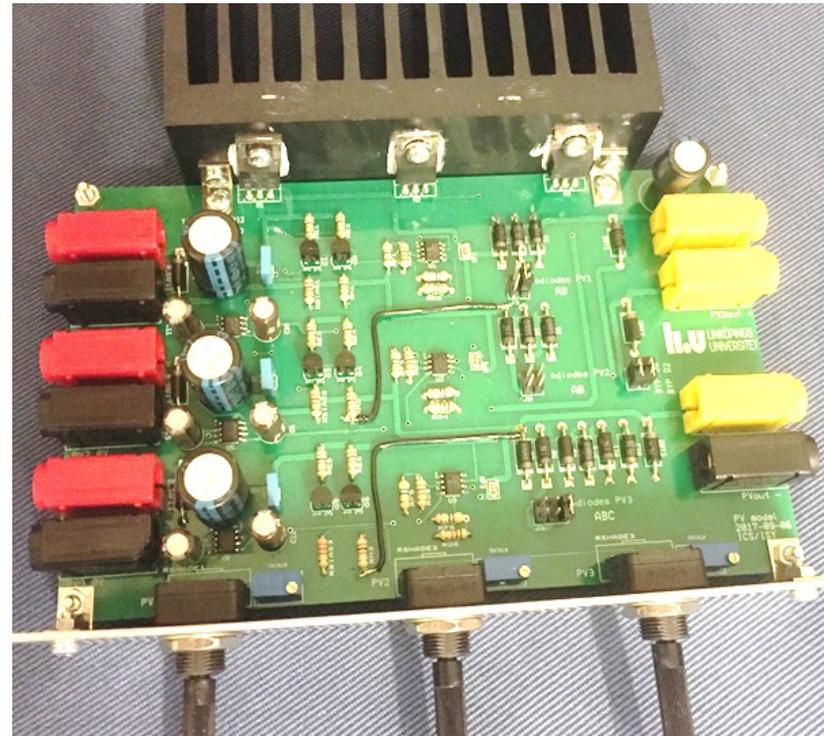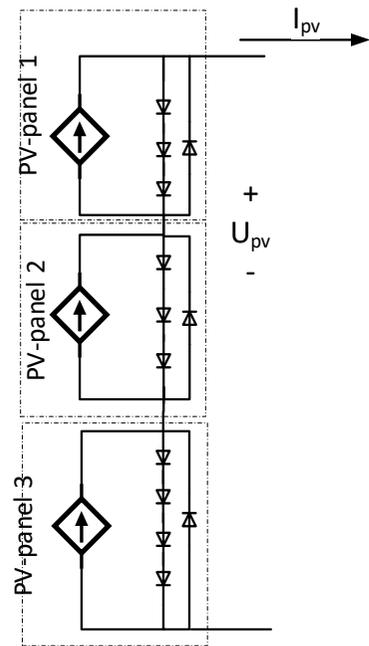



Partial shading

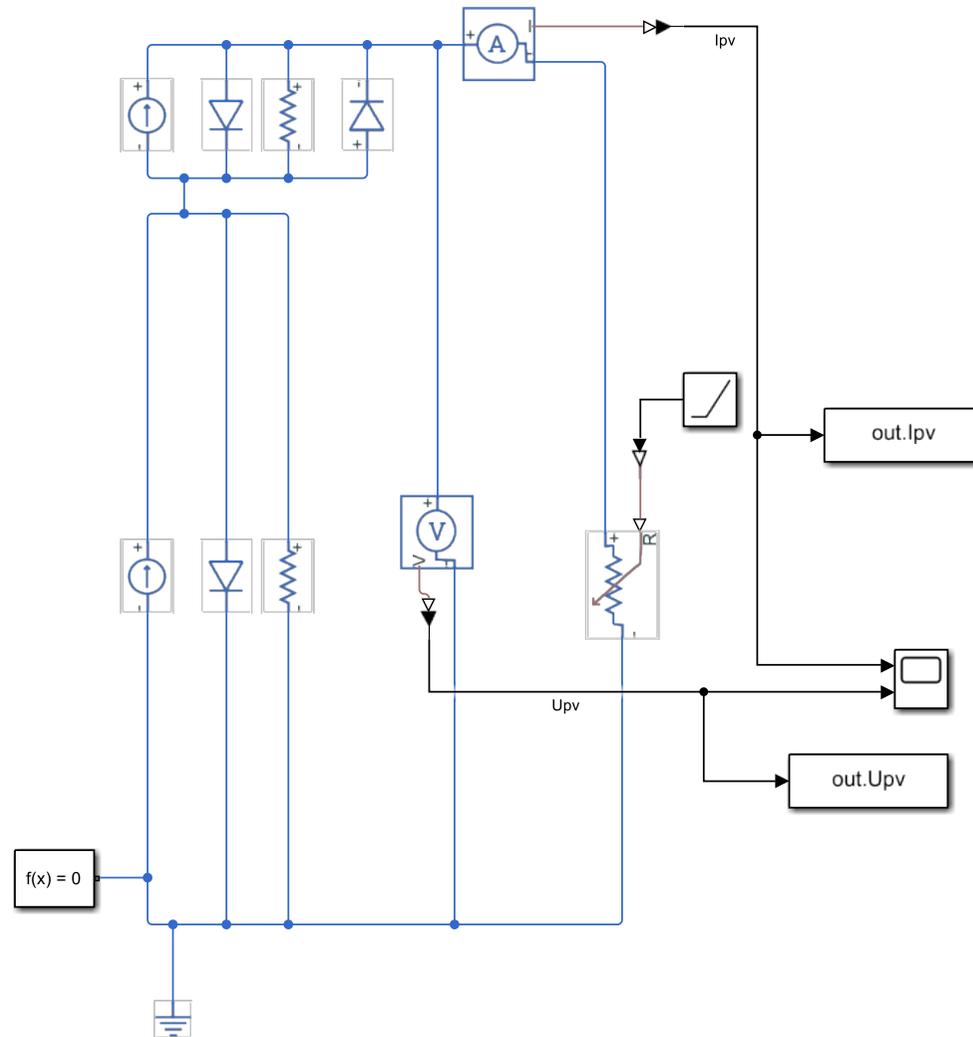

DC/DC Boost MPPT

Parameters for Perturb and Observe Algorithm:

(D = Boost converter duty cycle)

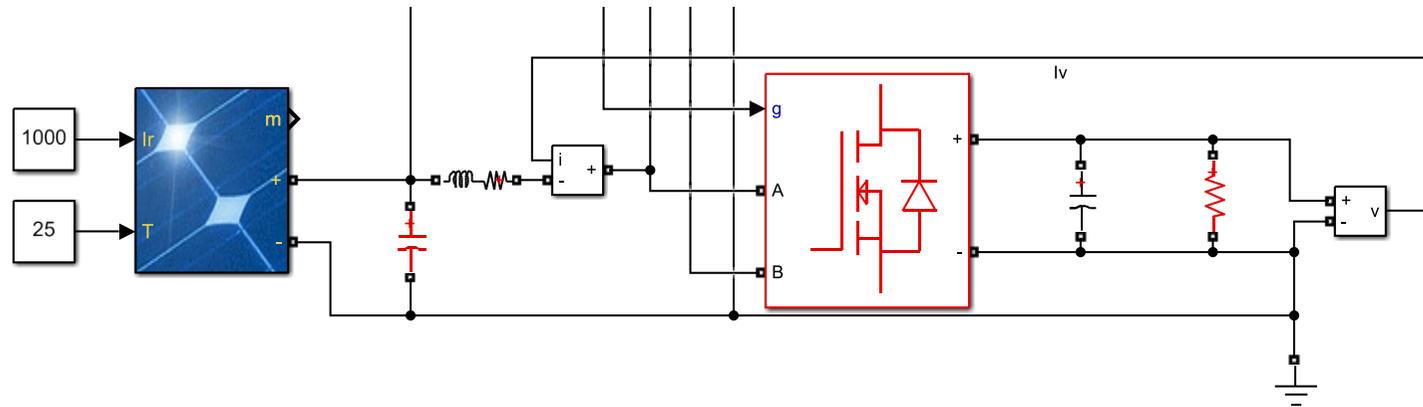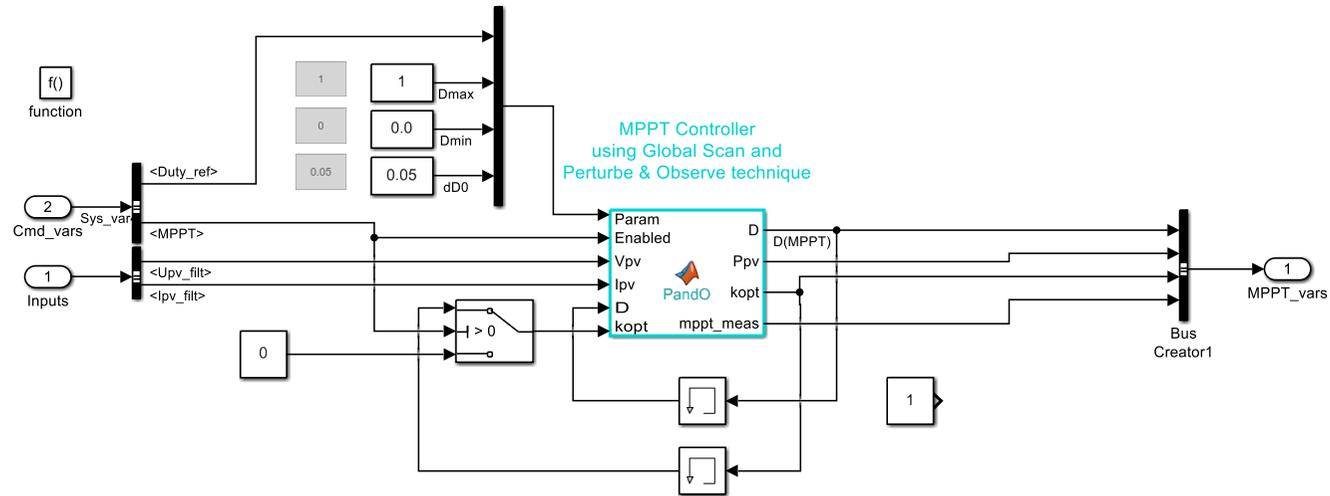

TSTE26
Lars Eriksson

www.liu.se